

Homework 3 Solutions

Due: Friday Sep 26, 5pm

Total for CS150/EE141: 90

Total for EE241A: 100

Note: For all questions, valid solutions may implement either Mealy or Moore machines unless the question specifies one or the other.

1. [10 pts] This solution has an external reset, as well as an internal "reset" to get the circuit ready to receive the next one-hot sequence. A valid answer could also assume, based on the wording of the question, that an external reset would be asserted between arriving one-hot sequences.

```
module onehot_to_bin(  
    input clk,  
    input rst,  
    input serial_in,  
    input in_valid,  
    output reg bin_out,  
    output reg out_valid);  
  
    // synchronous registers  
    reg [3:0] one_hot_reg;  
    reg [2:0] count;  
  
    // asynchronous regs  
    reg [3:0] next_one_hot_reg;  
    reg [2:0] next_count;  
  
    always @(posedge clk) begin  
        if(rst)  
            one_hot_reg <= 4'b0;  
            count <= 4'b0;  
        else begin  
            if(in_valid) begin  
                count <= next_count;  
                one_hot_reg <= next_one_hot_reg;  
            end  
        end  
    end
```

```

        end
    end

    always @(*) begin
        next_one_hot_reg = {one_hot_reg[2:0], serial_in};
        next_count = count + 1;
        if(count == 4) begin
            next_one_hot_reg = 4'b0;
            next_count = 3'b0;
            case(one_hot_reg)
                4'b0001: begin
                    out_valid = 1'b1;
                    bin_out = 2'b00;
                end

                4'b0010: begin
                    out_valid = 1'b1;
                    bin_out = 2'b01;
                end

                4'b0100: begin
                    out_valid = 1'b1;
                    bin_out = 2'b10;
                end

                4'b1000: begin
                    out_valid = 1'b1;
                    bin_out = 2'b11;
                end


                default: begin
                    out_valid = 1'b0;
                    bin_out = 2'b00;
                end
            endcase
        end
    end
endmodule

```

2. *[4 pts]* The case statement will infer a flat mux structure, while nested if-else will infer cascading logic.
3. *[16 pts total]*
 - Problem explicitly states that the machine does not return change. -4 pts overall for a working solution that returns change.

- Problem explicitly states that the solution cannot use a counter. -12 pts overall for any solution that uses a counter to simply keep track of the amount deposited.

(a) [8 pts]

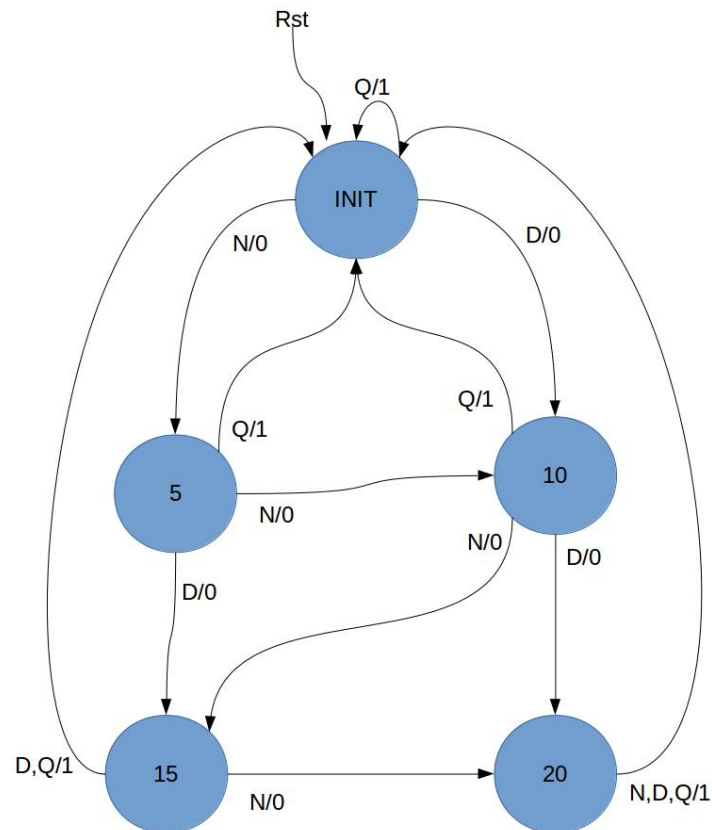

```

module vending_mealy(
    input clk,
    input rst,
    input quarter,
    input dime,
    input nickel,
    output reg dispense);

    localparam INIT = 3'd0;
    localparam FIVE = 3'd1;
    localparam TEN = 3'd2;
    localparam FIFTEEN = 3'd3;
  
```

```

localparam TWENTY = 3'd4;

reg [2:0] current_state;

always @(posedge clk) begin
    if(rst) begin
        current_state <= INIT;
        dispense <= 0;
    end else begin
        dispense <= 0;
        case(current_state)
            INIT: begin
                if(nickel)
                    current_state <= FIVE;
                else if(dime)
                    current_state <= TEN;
                else if(quarter) begin
                    current_state <= INIT;
                    dispense <= 1;
                end
            end
            FIVE: begin
                if(nickel)
                    current_state <= TEN;
                else if(dime)
                    current_state <= FIFTEEN;
                else if(quarter) begin
                    current_state <= INIT;
                    dispense <= 1;
                end
            end
            TEN: begin
                if(nickel)
                    current_state <= FIFTEEN;
                if(dime)
                    current_state <= TWENTY;
                else if(quarter)
                    current_state <= INIT;
                    dispense <= 1;
            end
            FIFTEEN: begin
                if(nickel)

```

```


        current_state <= TWENTY;
    else if(dime | quarter) begin
        current_state <= INIT;
        dispense <= 1;
    end
end

    TWENTY: begin
        if(nickel | dime | quarter) begin
            current_state <= INIT;
            dispense <= 1;
        end
    end

    default: current_state <= INIT;
endcase
end
end
endmodule

```

(b) [8 pts]

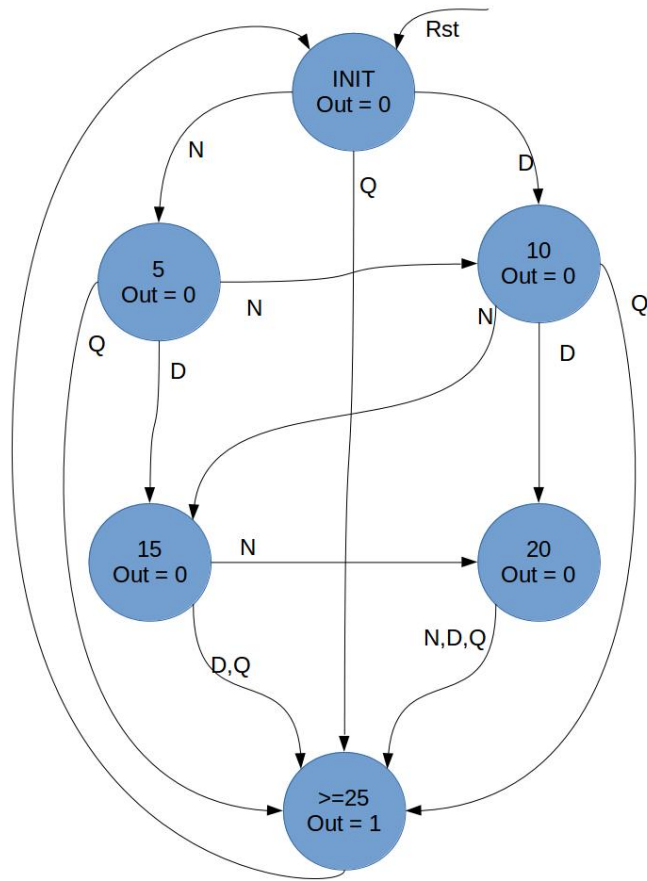

```

module vending_moore(
    input clk,
    input rst,
    input quarter,
    input dime,
    input nickel,
    output dispense);

    localparam INIT = 3'd0;
    localparam FIVE = 3'd1;
    localparam TEN = 3'd2;
    localparam FIFTEEN = 3'd3;
    localparam TWENTY = 3'd4;
    localparam TWENTYFIVE = 3'd5;

    reg [2:0] current_state;
    reg [2:0] next_state;
  
```

```

always @(posedge clk) begin
    if(rst)
        current_state <= INIT;
    else
        current_state <= next_state;
end

always @(*) begin
    case(current_state)
        INIT: begin
            if(nickel)        next_state = FIVE;
            else if(dime)     next_state = TEN;
            else if(quarter)  next_state = TWENTYFIVE;
            else               next_state = current_state;
        end

        FIVE: begin
            if(nickel)        next_state = TEN;
            else if(dime)     next_state = FIFTEEN;
            else if(quarter)  next_state = TWENTYFIVE;
            else               next_state = current_state;
        end

        TEN: begin
            if(nickel)        next_state = FIFTEEN;
            else if(dime)     next_state = TWENTY;
            else if(quarter)  next_state = TWENTYFIVE;
            else               next_state = current_state;
        end

        FIFTEEN: begin
            if(nickel)        next_state = TWENTY;
            else if(dime | quarter) next_state = TWENTYFIVE;
            else               next_state = current_state;
        end

        TWENTY: begin
            if(nickel | dime | quarter) next_state = TWENTY_FIVE;
            else next_state = current_state;
        end

        TWENTYFIVE:
            next_state = INIT;
    endcase
end

```

```

        default:
            next_state = INIT;
        endcase
    end

    assign dispense = current_state == TWENTYFIVE;

endmodule

```

4. [4 pts]

Four major fixes (1 pt each):

- Need to use `always@(posedge clk)` instead of `always@(*)`
- Need `rst` in the sensitivity list b/c it needs to be asynchronous
- Need to make use of the `en` input
- Need to use non-blocking instead of blocking assignments

```

module dff{
    input clk,
    input rst,
    input en,
    input d,
    output q};

    reg q_reg;
    assign q = q_reg;
    always @(posedge clk or posedge rst) begin
        if(rst)
            q_reg <= 1'b0;
        else begin
            q_reg <= en ? d : q_reg;
        end
    end
endmodule

```

5. [8 pts total]

(a) [4 pts]

```

module fsm(
    input clk,
    input in,
    output out);

    reg [1:0] PS;

```



```

reg [1:0] NS;


always @(posedge clk) begin
    PS <= NS;
end

assign NS[0] = (~in & PS[1]) | (in & ~PS[0]);
assign NS[1] = PS[0] ^ PS[1];
assign out = ~PS[0] | ~PS[1];

endmodule

```

(b) [4 pts]

 

6. [4 pts] Half credit if the solution works but doesn't use a generate statement, since the question explicitly asks you to use a generate statement.

```

module edge_detect #(
    parameter delay = 1;
)
(
    input clk;
    input rst;
    input in;

```

```

    output out;
);

reg prev_in;
reg rise;
reg [delay-1:0] delay_chain;

genvar i;

generate
    for(i = 1; i < delay; i = i + 1)
        begin: gen_delay
            always @(posedge clk) begin
                delay_chain[i] <= delay_chain[i-1];
            end
        end
    endgenerate


always @(posedge clk) begin
    if(rst) begin
        prev_in <= 1'b0;
        rise <= 1'b0;
    end else begin
        delay_chain[0] <= rise;
        prev_in <= in;
        if(~prev_in && in)
            rise <= 1'b1;
        else
            rise <= 1'b0;
    end
end
endmodule

```


7. [24 pts total]

For each part of this problem, -2 pts for excessively complex solutions.

(a) [4 pts]

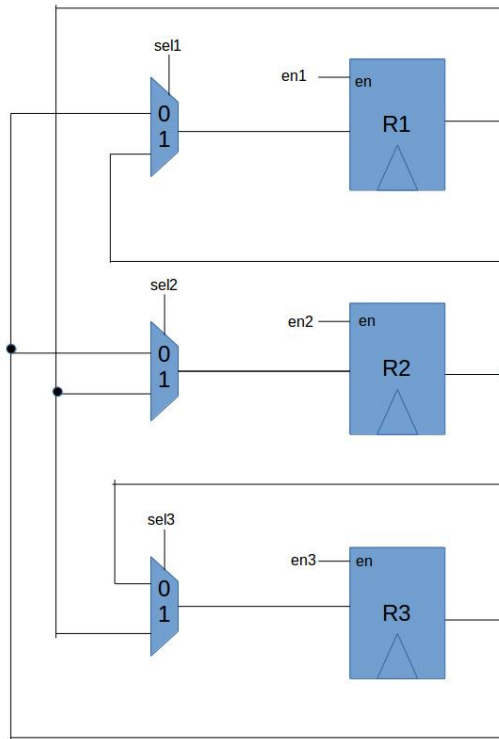

(b) [4 pts]

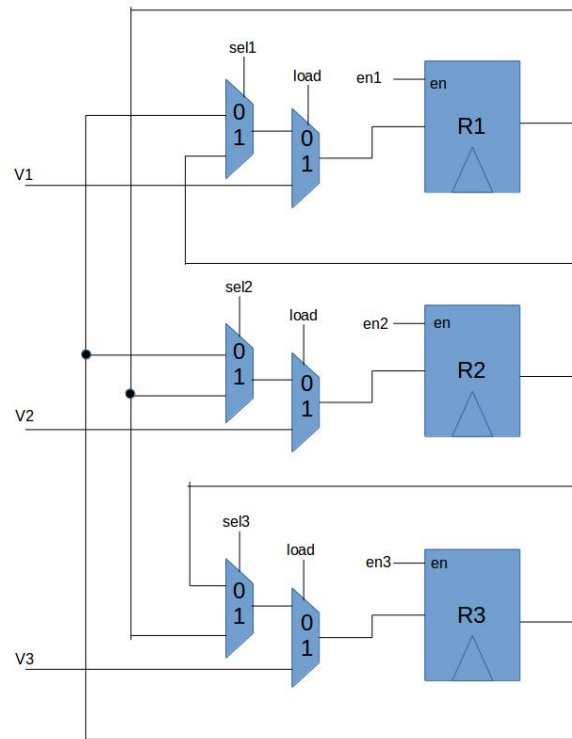

(c) [4 pts]

```

module swapper_dpath(
    input clk,
    input v1,
    input v2,
    input v3,
    input sel1,
    input sel2,
    input sel3,
    input en1,
    input en2,
    input en3,
    input load,
    output reg r1,
    output reg r2,
    output reg r3);

```

```


always @(posedge clk) begin
    if(en1) r1 <= next_r1;
    if(en2) r2 <= next_r2;
    if(en3) r3 <= next_r3;
end

always @(*) begin
    next_r1 = sel1 ? r2 : r3;
    next_r1 = load ? v1 : next_r1;
    next_r2 = sel2 ? r1 : r3;
    next_r2 = load ? v2 : next_r2;
    next_r3 = sel3 ? r1 : r2;
    next_r3 = load ? v3 : next_r3;
end

endmodule

```

 - (d) [4 pts] To swap R1 and R2, you need to make sure "load" is deasserted. Then assert "sel1" and "sel2" and "en1" and "en2" all at the same time. On the next clock edge, the values will be swapped.
- (e) [4 pts] In first state, use a comparator to determine if R1 is less than R2. If R1 is less, then swap R1 and R2 and transition to 2nd state. In this state, compare R1 to R3, and swap if R1 is less and transition to 3rd state. Finally, compare R2 and R3, and swap if R2 is less. Then transition to the "DONE" state and stay there until reset.



- (f) [4 pts]

```

module swapper_control(
    input clk,
    input rst,
    input r1,
    input r2,
    input r3,
    output reg sel1,
    output reg sel2,
    output reg sel3,
    output reg en1,

```

```

output reg en2,
output reg en3,
output done);

localparam R1R2 = 2'd0;
localparam R1R3 = 2'd1;
localparam R2R3 = 2'd2;
localparam DONE = 2'd3;

always @(posedge clk) begin
    if(rst)
        current_state <= R1R2;
    else
        current_state <= next_state;
end

always @(*) begin
    sel1 = 0;
    sel2 = 0;
    sel3 = 0;
    en1 = 0;
    en2 = 0;
    en3 = 0;
    case(current_state)
        R1R2: begin
            next_state = R1R3;
            if(r1 < r2) begin
                sel1 = 1;
                sel2 = 1;
                en1 = 1;
                en2 = 1;
            end
        end
        R1R3: begin
            next_state = R2R3;
            if(r1 < r3) begin
                sel1 = 0;
                sel3 = 1;
                en1 = 1;
                en3 = 1;
            end
        end
        R2R3: begin

```

```

        next_state = DONE;
        if(r2 < r3) begin
            sel2 = 0;
            sel3 = 0;
            en2 = 1;
            en3 = 1;
        end
    end

    DONE:
        next_state = current_state;

endcase
end

assign done = current_state == DONE;

endmodule


```

8. [20 pts total]

(a) [7 pts]

Any valid encoding receives full credit. Here we use one-hot encoding to simplify logic:

STATE		ENCODING
INIT		00001
1		00010
10		00100
101		01000
1010		10000

 


(b) [4 pts]

x	curr_state	next_state
<hr/>		
0	00001	00001
0	00010	00100
0	00100	00001
0	01000	10000
0	10000	00001
1	00001	00010
1	00010	00010
1	00100	01000
1	01000	00010
1	10000	01000

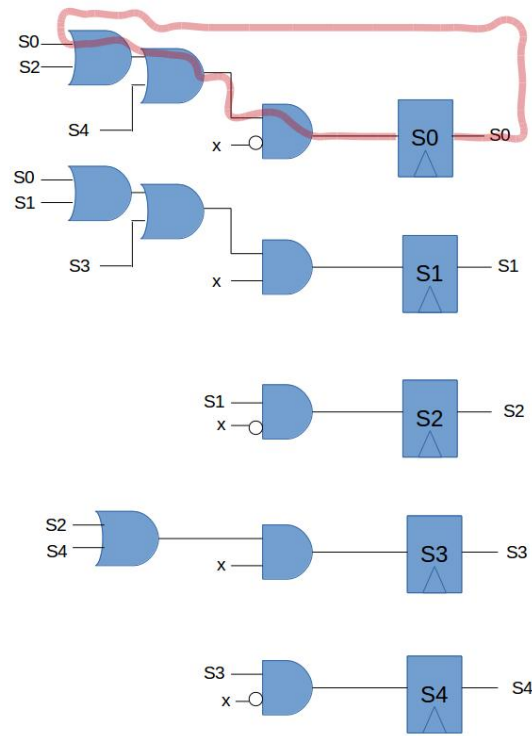(c) [6 pts]

For simplicity, not all wires are drawn. Register outputs on the right (S0, S1,..., S4) correspond to the nodes on the left with the same label. The only input is x .



(d) [3 pts]

$$T_{clk} > T_{clk-to-q} + T_{CL} + T_{setup}$$

$$T_{clk} > 1ns + 3ns + 0.8ns$$

$$T_{clk} > 4.8ns$$

9. [10 pts]

Any solution that recognizes that you only need to keep track of the number mod 5 should receive at least 6 pts for the problem. The other 4 points is for a correct implementation.

