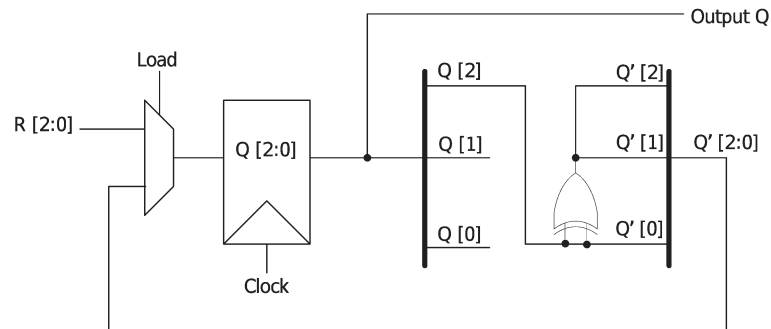


2. (a)

[6]



(b)

[2]

The generator always outputs 000 after the first cycle.

Cycle	Q[2], Q[1], Q[0]
0	001
1	000
2	000
3	...

3.

[6]

```

module counter(
    input clk,
    input reset,
    input up_down,
    output [7:0] count
);
    reg [7:0] cnt;

    assign count = cnt;

    always@(posedge clk) begin

        if(reset)
            cnt <= 8'd0;
        else if(up_down == 0)
            cnt <= cnt + 1;
        else
            cnt <= cnt - 1;
    end

endmodule

```

4. (a) [2]

$$Y = a\bar{b}\bar{c} + a\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + b\bar{c}$$

(b) [4]

$$Y = a\bar{b}\bar{c} + a\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + b\bar{c}$$

$$Y = a\bar{b}(\bar{c} + c) + \bar{a}b(\bar{c} + c) + b\bar{c}$$

$$Y = a\bar{b} + \bar{a}b + b\bar{c}$$

$$Y = \bar{b}(a + \bar{a}) + b\bar{c}$$

$$Y = \bar{b} + b\bar{c}$$

5. (a) 3-bit input is a,b,c. Output is y. [4]

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b) [8]

$$Y = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$

$$Y = bc(\bar{a} + a) + a\bar{b}c + ab\bar{c}$$

$$Y = bc + a\bar{b}c + ab\bar{c}$$

$$Y = b(c + a\bar{c}) + a\bar{b}c$$

$$Y = b(c + a) + a\bar{b}c \text{ (by elimination theorem)}$$

$$Y = bc + ab + a\bar{b}c$$


$$Y = bc + a(b + \bar{b}c)$$

$$Y = bc + a(b + c) \text{ (by elimination theorem)}$$

$$Y = bc + ab + ac$$

 (c) [2]

$$y = (a + b + c)(a + b + \bar{c})(a + \bar{b} + c)(\bar{a} + b + c)$$



6.

[12]

		w			
cd	ab	00	01	11	10
	00	0	0	-	1
	01	0	0	-	0
	11	0	1	-	-
	10	0	0	-	-

$$W = bcd + a\bar{d}$$

		x			
cd	ab	00	01	11	10
	00	0	1	-	0
	01	0	1	-	0
	11	1	0	-	-
	10	0	1	-	-

$$X = b\bar{c} + b\bar{d} + \bar{b}cd$$

		y			
cd	ab	00	01	11	10
	00	0	0	-	0
	01	1	1	-	0
	11	0	0	-	-
	10	1	1	-	-

$$Y = \bar{a}cd + c\bar{d}$$

		z			
cd	ab	00	01	11	10
	00	1	1	-	1
	01	0	0	-	0
	11	0	0	-	-
	10	1	1	-	-

$$Z = \bar{d}$$

7. (a)

[12]

		\bar{x}			
c	ab	00	01	11	10
0		0	1	1	0
1		0	0	1	1

$$X = b\bar{c} + ac$$

		\bar{y}			
c	ab	00	01	11	10
0		0	1	1	0
1		1	1	0	0

$$Y = b\bar{c} + \bar{a}c$$

		\bar{z}			
c	ab	00	01	11	10
0		1	0	1	0
1		1	0	1	0

$$Z = \bar{a}\bar{b} + ab$$

(b) Note: x,y,z is equivalent to cnt[2], cnt[1], cnt[0].

[5]

```

module counter(
    input clk,
    output reg [2:0] cnt
);
    always@(posedge clk) begin
        cnt[2] <= (cnt[1] & !cnt[0]) | (cnt[2] & cnt[0]);
        cnt[1] <= (cnt[1] & !cnt[0]) | (!cnt[2] & cnt[0]);
        cnt[0] <= (!cnt[2] & !cnt[1]) | (cnt[2] & cnt[1]);
    end
endmodule

```

8.

[7]

```

module serial_to_parallel(
    input clk,
    input sin,
    input shift_in,
    input load_pout,
    output reg [3:0] pout
);
    reg [3:0] temp_pout;

    always@(posedge clk) begin

```

```

        if(shift_in)
            temp_pout <= {temp_pout[2:0], sin};

        if(load_pout)
            pout <= temp_pout;
    end

endmodule

```

9. (a) There are three critical paths. [3]

Path 1: from output of R1, through G2, G4, G1, to input of R1.

Path 2: from output of R1, through G3, G4, G1, to input of R2.


Path 3: from output of R2, through G3, G4, G1, to input of R1.

- (b) [4]


$$\begin{aligned}
 \text{Max delay} &= T_{\text{clk-q, max}} + 3 \times T_{\text{gate, max}} + T_{\text{setup}} \\
 &= 60ps + 3 \times 100ps + 50 \\
 &= 410ps \\
 F_{\text{max}} &= \frac{1}{410ps} = 2.44\text{GHz}
 \end{aligned}$$

- (c) No. The shortest path in the circuit is R2 through G1 to R1. Minimum clk-to-q + minimum gate delay = 120ps. This is larger than the hold time of 45ps, hence hold time will not be violated. [2]

 
10. **For EE241A only:** We can build AND, OR and NOT gates as follows: [10]



$Y = a \text{ AND } b$

 

$Y = a \text{ OR } b$

 

$Y = \text{NOT } a$

To build a NAND gate: connect NOT to output of AND.

To build a NOR or XOR gate: connect NOT gates to the inputs/outputs of an OR gate.