 


Figure 1: Diagram for question 2

3. For a carry-select adder, assume that the select groups are all of the same number of bits, and the carry delay through a full-adder cell is equal to the delay of a 2-to-1 mux.
  - (a) What is the optimal size select group for a 32-bit adder?
  - (b) What is the optimal size select group for a 64-bit adder?
4.
  - (a) Draw a wallace tree for a  $5 \times 5$  multiplier, using Full Adder, and Half Adder cells
  - (b) Add one pipeline stage to improve the throughput as much as possible. What is the new critical path?
5. Make a table comparing array, sequential, and bit-serial multipliers with respect to cost in terms of FA cells, cost in terms of FFs, and delay, all as a function of  $n$ , the number of bits in the inputs. Use “big O” notation.

6. For EE241A only:

- (a) Shown below is a static CMOS implementation of a gate that computes the carry-out at a particular bit position. If the P signal fed into the gate is calculated using  $P = A + B$  (instead of  $P = A \oplus B$ , which is usually the case) would the output of this gate still be correct? Why or why not? If not, suggest a modification that gives the right output.



- (b) Show the static CMOS implementation of a gate that computes the sum at a particular bit position ( $S = P \oplus C_{in}$ ). Again, if the P signal fed into the gate is calculated using  $P = A + B$ , is the output of the gate correct? Why or why not? If not, suggest a modification that gives the right output.
- (c) The gate shown below is a Manchester carry chain implementation that computes the carry-out for two bit positions. Does this gate give the correct output if  $P = A + B$ ? Why or why not?

