

# Discussion #5

10/3/2014 and 10/6/2014

# Review


- Week 1: Intro: EE141 vs. CS150
- Week 2: RTL (Verilog)
- Week 3: Sequential+Combinational, Boolean
- Week 4: Finite State Machines
- Week 5: CMOS + hand models
- **Week 6: Wires + power/energy**

# For example

- Week 1: Intro: EE141 vs. CS150
- Week 2: RTL (Verilog)
- Week 3: Sequential +Combinational, Boolean
- Week 4: Finite State Machines
- Week 5: CMOS + hand models
- **Week 6: Wires + power/energy**
- Design a chip that detects the sequence 3 or ore 1s in a row (out=1 if detected)
- -> **Draw FSM**
- -> **Describe in Verilog (Mealy vs. Moore?)**
- -> **Write table (current state/input | next state/output)**
- -> **Next state logic/K-map**
- -> **Implement at gate-level**
- -> **Gate-level timing**
- -> **Transistor-level timing**
- -> **How would you do this in lab?**

# Practice problem

- Elmore delay

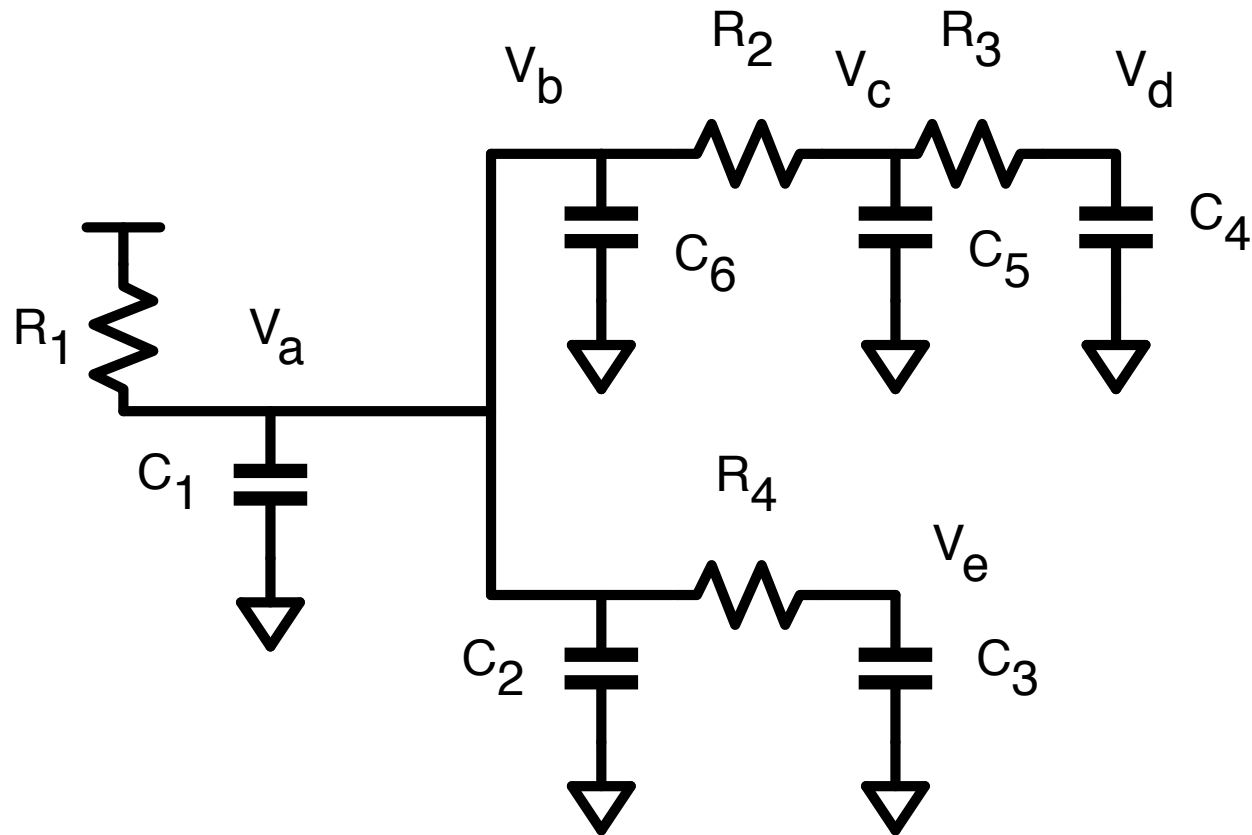


# Answer

- Short any resistor not on the desired path:
- Va to Vd:  $\tau = R1(C1+C2+C3+C6) + (R1+R2)(C5) + (R1+R2+R3)(C4)$
- Then delay is  $0.69\tau$

# Practice Problem

- Energy: Energy when input 0→1.2

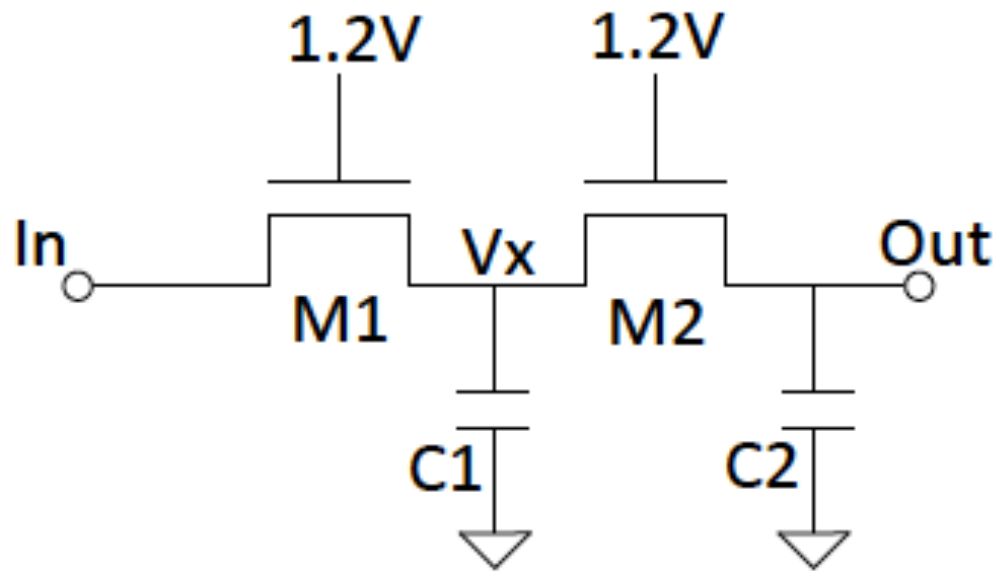

For this problem, you can assume an ideal pulse at the input and  $C_1 = C_2 = 50\text{fF}$ . Ignore leakage and device capacitance. The nominal supply voltage is 1.2V,  $V_{TH} = V_{TH,N} = |V_{TH,P}| = 0.2\text{V}$  and  $R_{ON,N} = R_{ON,P} = R$ .

# Answer

Source is always the lower potential (for NMOS...or higher potential for PMOS)  
NMOS can only pull up to  $V_{dd} - V_{th}$   
PMOS can only pull down to  $V_{th}$

Both capacitors get charged from 0 to 1V. Note that the supply in this case is the input source. Therefore the total charge drawn from the supply is:

$$Q = C_1 \cdot \Delta V_1 + C_2 \cdot \Delta V_2 = 2C_1(V_{fin} - V_{init})$$

$$E_{0 \rightarrow 1} = Q \cdot V_{SUP} = 2C_1(V_{fin} - V_{init})V_{SUP} = 2 \cdot 50 \text{ fF} \cdot 1V \cdot 1.1V = 110 \text{ fJ}$$

$$E_{C1,stored} = E_{C2,stored} = \frac{1}{2}C_1V_{out,fin}^2 = \frac{1}{2}50 \text{ f}(1V)^2 = 25 \text{ fJ}$$

$$E_{dis} = E_{0 \rightarrow 1} - E_{stored} = 110 \text{ fJ} - 25 \text{ fJ} - 25 \text{ fJ} = 60 \text{ fJ}$$