



# **CS150 Discussion 3**

**Simon Scott**

# Coding Guidelines

1. When modeling **sequential** logic, use **nonblocking** assignments.
2. When modeling **latches**, use **nonblocking** assignments.
3. When modeling **combinational** logic with an **always** block, use **blocking** assignments.
4. When modeling **both sequential and combinational** logic within the same **always** block, use **nonblocking** assignments.
5. **Do not mix blocking and nonblocking** assignments in the same **always** block.
6. **Do not** make assignments to the same variable from more than one **always** block.

# *Blocking vs Non-blocking*



```
module m_nb (  
    input clk,  
    input in,  
    output [7:0] cout  
);  
    reg [7:0] accum;  
    reg [7:0] accum_d;  
  
    always@(posedge clk) begin  
        accum <= accum + in;  
        accum_d <= accum;  
        cout <= accum_d;  
    end  
endmodule
```





```
module m_b (  
    input clk,  
    input in,  
    output [7:0] cout  
);  
    reg [7:0] accum;  
    reg [7:0] accum_d;  
  
    always@(posedge clk) begin  
        accum = accum + in;  
        accum_d = accum;  
        cout = accum_d;  
    end  
endmodule
```

# Examples of using (non)-blocking assign

```
module statemachine (  
    input clk,  
    input rst,  
    input in_a,  
    output out_a  
);  
    reg [1:0] curr_state;  
    reg [1:0] next_state;
```

```
endmodule
```

```
always @(posedge clk)  
    if (rst) curr_state  STATE_0;  
    else curr_state  next_state;
```

```
always @(*)  
    case (curr_state)  
  
        STATE_0: if (in_a) begin  
            out_a  1'b1;  
            next_state  STATE_1;  
        end  
        else begin  
            out_a  1'b0;  
            next_state  STATE_0;  
        end  
  
        STATE_1: if (in_a) begin  
            .....  
        end  
        default: ...  
  
    endcase
```

```
end  
end
```

# *Boolean Algebra*

Simplify:  $ab + aa' + bc + ab' + c$

DeMorgan's Law:

$$(x + y + z + \dots)' = x'y'z'$$

$$(x y z \dots)' = x' + y' + z'$$

Simplify:  $\overline{(\bar{a} + \bar{b}) * (a + \bar{b}) * c}$

Simplify:  $Y = \overline{A} \overline{B} * \overline{C} * \overline{D} + A * \overline{B} * \overline{C} + A * \overline{B} * C * \overline{D} + ABD + \overline{A} \overline{B} * C * \overline{D}$

# *Truth Tables*

Circuit has a 4-bit input  $\{A_3, A_2, A_1, A_0\}$ , representing a binary number.

Output  $P = 1$  if  $A$  is prime or 15; otherwise  $P = 0$ .

Note: 0 and 1 are not prime,

a.) Draw the truth table

b.) Write SoP and simplify using multi-level logic

Hint: factorize!

c.) Write the first 4 terms of the PoS expression

d.) Use K-maps to find a simplified expression for  $P$

# Karnaugh Maps

Simplify using K-map:



A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

# Using NAND Gates

*DeMorgan's Law Review:*



$$(a + b)' = a' b'$$

$$a + b = (a' b')'$$

  

$$(a b)' = a' + b'$$

$$(a b) = (a' + b')'$$

  

*Convert to NANDs:*

$$f = a(b + cd) + bc'$$

