


# EE141 – Discussion #3

Nathan Narevsky


9/19/2014 and 9/22/2014

# Mealy vs. Moore

## Mealy Model

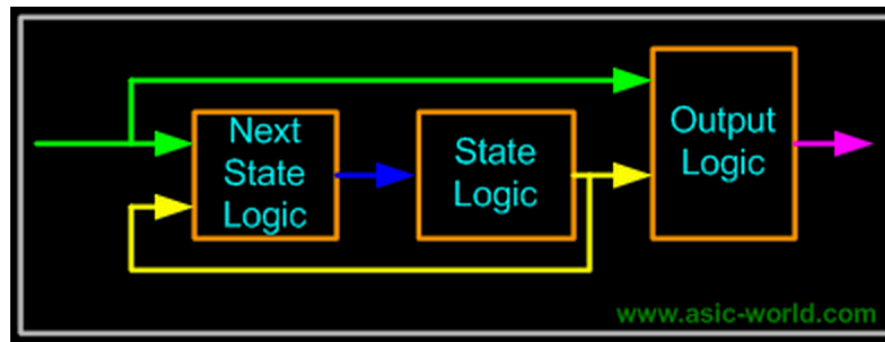

## Moore Model

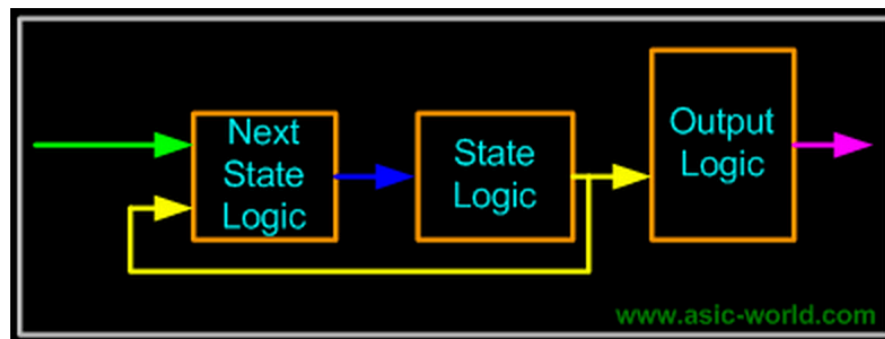

# FSM Comparison

## Solution A


### Moore Machine

- output function only of PS
- maybe more states (why?)
- synchronous outputs
  - no glitches
  - one cycle “delay”
  - full cycle of stable output

## Solution B
 
### Mealy Machine

- output function of both PS & input
- maybe fewer states
- asynchronous outputs
  - if input glitches, so does output
  - output immediately available
  - output may not be stable long enough to be useful (below):



If output of Mealy FSM goes through combinational logic before being registered, the CL might delay the signal and it could be missed by the clock edge.

# More on Generate Loop

Permits variable declarations, modules, user defined primitives, gate primitives, continuous assignments, initial blocks and always blocks to be instantiated multiple times using a for-loop.

```
// Gray-code to binary-code converter
```

```
module gray2bin1 (bin, gray);
```

```
    parameter SIZE = 8;
```

```
    output [SIZE-1:0] bin;
```

```
    input  [SIZE-1:0] gray;
```

```
    genvar i;
```

```
    generate for (i=0; i<SIZE; i=i+1) begin:bit
```

```
        assign bin[i] = ^gray[SIZE-1-i];
```

```
    end endgenerate
```

```
endmodule
```

variable exists only in the specification - not in the final circuit.

Keywords that denotes synthesis-time operations


For-loop creates instances of assignments

Loop must have constant bounds

generate if-else-if based on an expression that is deterministic at the time the design is synthesized.

generate case : selecting case expression must be deterministic at the time the design is synthesized.

# Example - Parallel to Serial Converter

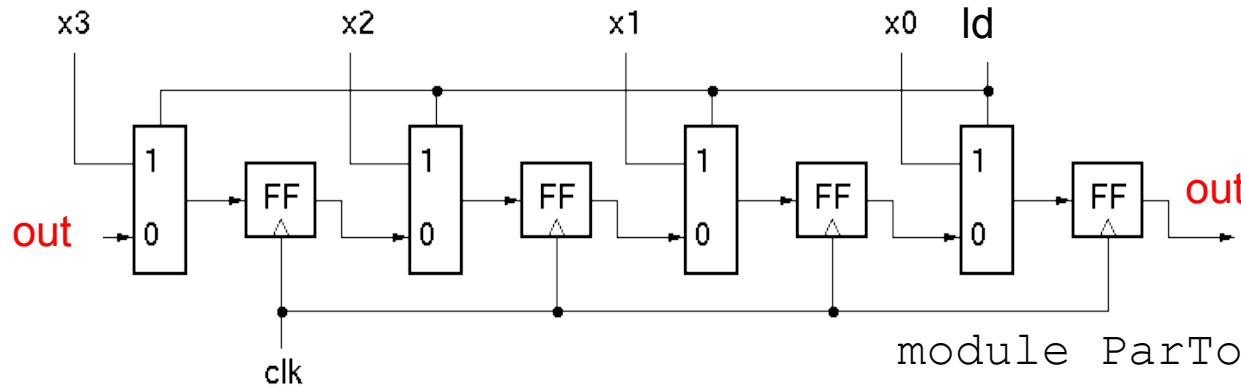

```
module ParToSer(ld, X, out, clk);
    input [3:0] X;
    input ld, clk;
    output out;
```

```
    reg [3:0] Q;
    wire [3:0] NS;
```

```
    assign NS =
        (ld) ? X : {Q[0], Q[3:1]};
```

```
    always @ (posedge clk)
        Q <= NS;
```

```
    assign out = Q[0];
```

```
endmodule
```

Specifies the  
muxing with  
"rotation"

forces Q register (flip-flops) to be  
rewritten every cycle

connect output

# Parameterized Version

Parameters give us a way to generalize our designs. A module becomes a “generator” for different variations. Enables design/module reuse. Can simplify testing.

```
parameter N = 4;
```

Declare a parameter with default value.

Note: this is not a port. Acts like a “synthesis-time” constant.

```
ParToSer #(.N(8))  
ps8 ( ... );
```

```
ParToSer #(.N(64))  
ps64 ( ... );
```

Overwrite parameter N at instantiation.

```
module ParToSer(ld, X, out, CLK);
```

```
input [N-1:0] X;
```

```
input ld, clk;
```

```
output out;
```

```
reg out;
```

```
reg [N-1:0] Q;
```

```
wire [N-1:0] NS;
```

Replace all occurrences of “3” with “N-1”.

```
assign NS =
```

```
(ld) ? X : {Q[0], Q[N-1:1]};
```

```
always @ (posedge clk)
```

```
Q <= NS;
```

```
assign out = Q[0];
```

```
endmodule
```

# Incomplete Triggers

Leaving out an input trigger usually results in latch generation for the missing trigger.

```
module and_gate (out, in1, in2);  
    input      in1, in2;  
    output     out;  
    reg        out;
```

in2 not in always sensitivity list.

```
    always @(in1) begin  
        out = in1 & in2;  
    end  
  
endmodule
```

A latched version of in2 is synthesized and used as input to the and-gate, so that the and-gate output is not always sensitive to in2.

Easy way to avoid incomplete triggers for combinational logic is with: `always @*`

# Example: Ripple Carry Adder

```
module ripple_adder (  
    input [15:0] A,  
    input [15:0] B,  
    output [16:0] Sum  
);  
  
wire [16:0] carry;  
  
genvar i;  
generate for (i=0; i < 16; i=i+1) begin:foo  
    full_adder u0 (.A(A[i]), .B(B[i]), .Cin(carry[i]), .Sum(Sum[i]), .Cout(carry[i+1]));  
end endgenerate  
  
assign Sum[16] = carry[16];  
  
endmodule
```




# Parameterized Ripple Carry Adder

Parametrized version:

```
module ripple_adder #(parameter NUM_BITS = 16 ) (  
    input [NUM_BITS-1:0] A,  
    input [NUM_BITS-1:0] B,  
    output [NUM_BITS:0] Sum  
);  
  
wire [NUM_BITS:0] carry;  
  
genvar i;  
generate for (i=0; i < NUM_BITS; i=i+1) begin:foo  
    full_adder u0 (.A(A[i]), .B(B[i]), .Cin(carry[i]), .Sum(Sum[i]), .Cout(carry[i+1]));  
end endgenerate  
  
assign Sum[NUM_BITS] = carry[NUM_BITS];  
  
endmodule
```

# Pattern Detection - 1101

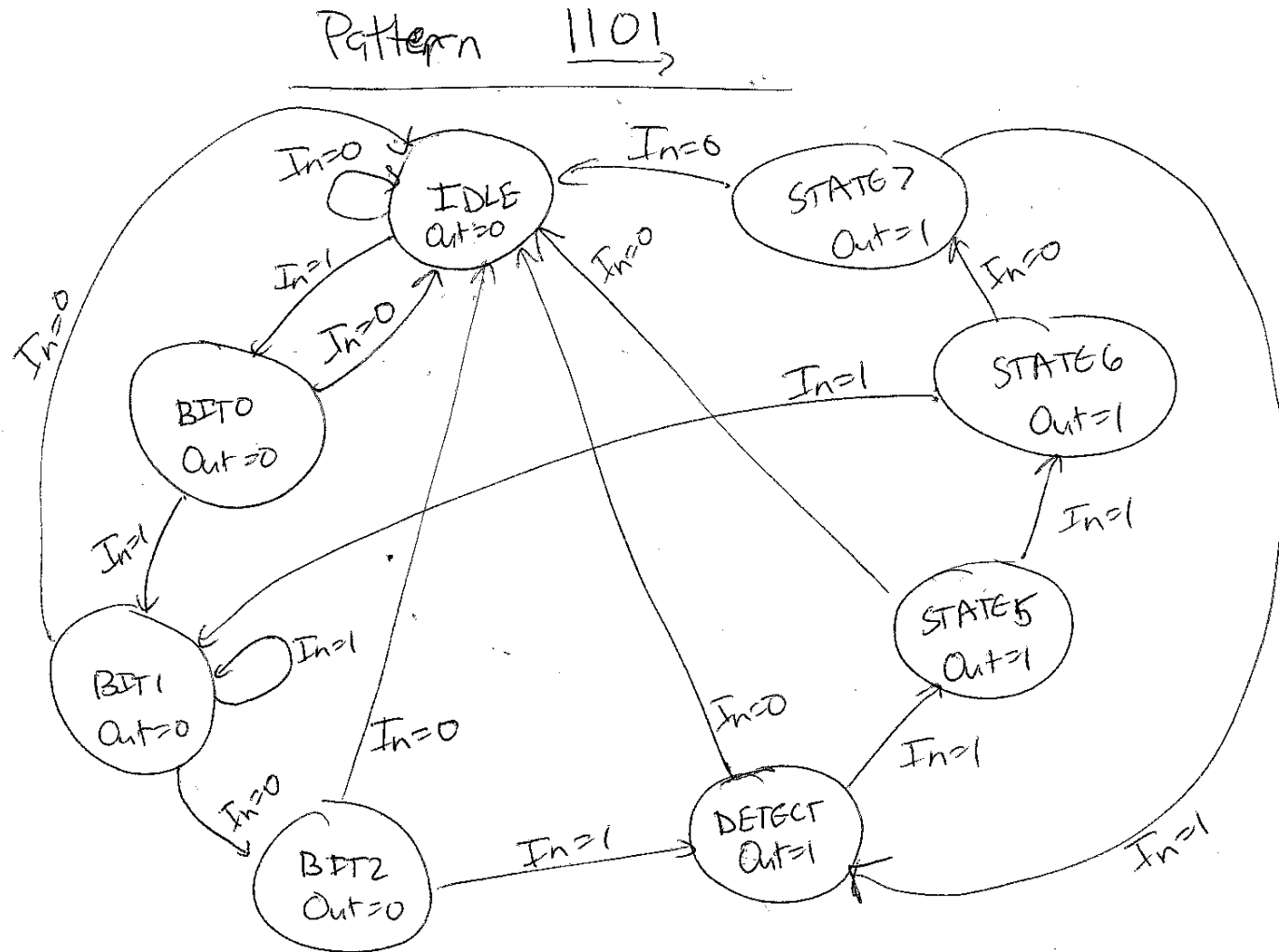

# Verilog Implementation

```
1101 Pattern Detector:
module pattern_detector (
    input In, clk,
    output Out
);
```

```
parameter IDLE = 3'b000,
    BIT0 = 3'b001,
    BIT1 = 3'b010,
    BIT2 = 3'b011,
    DETECT = 3'b100,
    STATE5 = 3'b101,
    STATE6 = 3'b110,
    STATE7 = 3'b111;
```

```
reg [2:0] state, next_state;
```

```
always @(posedge clk) begin
    state <= next_state;
end
```

```
always @(*) begin
    case(state)
    IDLE: begin
        Out <= 0;
        next_state <= In ? BIT0 : IDLE;
    end
    BIT0: begin
        Out <= 0;
```

```
        next_state <= In ? BIT1 : IDLE;
    end
    BIT1: begin
        Out <= 0;
        next_state <= In ? BIT1 : BIT2;
    end
    BIT2: begin
        Out <= 0;
        next_state <= In ? DETECT : IDLE;
    end
    DETECT: begin
        Out <= 1;
        next_state <= In ? STATE5 : IDLE;
    end
    STATE5: begin
        Out <= 1;
        next_state <= In ? STATE6 : IDLE;
    end
    STATE6: begin
        Out <= 1;
        next_state <= In ? BIT1 : STATE7;
    end
    STATE7: begin
        Out <= 1;
        next_state <= In ? DETECT : IDLE;
    end
    endcase
end
endmodule
```

# References

- [http://www.sunburst-design.com/papers/CummingsSNUG2003SJ\\_SystemVerilogFSM.pdf](http://www.sunburst-design.com/papers/CummingsSNUG2003SJ_SystemVerilogFSM.pdf)
- <http://www.asic-world.com/>