




CS150 - EE141/241A
Fall 2014

Digital Design and Integrated Circuits


Instructors:
John Wawrzynek and Vladimir Stojanovic

Lecture 8

Outline

 

 
- ❑ Digital abstraction
- ❑ CMOS abstraction
- ❑ Switch logic



Digital abstraction

Noise and Digital Systems



- ❑ Circuit needs to work despite “analog” noise
 - Digital gates can reject noise
 - This is actually how digital systems are defined
- ❑ Digital system is one where:
 - Discrete values mapped to analog levels and back
 - All the elements (gates) can reject noise
 - For “small” amounts of noise, output noise is less than input noise
 - Thus, for sufficiently “small” noise, the system acts as if it was noiseless

 


Noise Rejection

- To see if a gate rejects noise
 - Look at its DC voltage transfer characteristic (VTC)
 - See what happens when input is not exactly 1 or 0

  - Ideal digital gate:
 - Noise needs to be larger than $V_{DD}/2$ to have any effect on gate output





The Voltage Transfer Characteristic

 


$$\begin{aligned} V_{OH} &= f(V_{OL}) \\ V_{OL} &= f(V_{OH}) \\ V_M &= f(V_M) \end{aligned}$$

Voltage Mapping

  


Definition of Noise Margins

 


Noise margin high:
 $NM_H = V_{OH} - V_{IH}$

Noise margin low:
 $NM_L = V_{IL} - V_{OL}$

 Gate Output (Stage M) \longrightarrow Gate Input (Stage M+1)




 


CMOS abstraction

CMOS Devices

 - ❑ MOSFET (Metal Oxide Semiconductor Field Effect Transistor).





 The gate acts like a capacitor. A high voltage on the gate attracts charge into the channel. If a voltage exists between the source and drain a current will flow. In its simplest approximation, the device acts like a switch.




MOS Transistor as a Switch

  
An MOS Transistor \longleftrightarrow A Switch!



ON/OFF Switch Model of MOS Transistor

 


A More Realistic Switch

 


A Logic Perspective

NMOS Transistor

 


$Y=Z$ if $X=1$


A Complementary Switch

 


$Y=Z$ if $X=0$

 

PMOS Transistor

 

The Switch Inverter


 


$$X = 1 \quad out = 0$$

$$X = 0 \quad out = 1$$


The Switch Inverter

First-Order DC Analysis

  


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$


The CMOS Inverter: A First Glance

 

Simulated Inverter VTC (Spice)

 

 - ☐ $V_{OH} = 2.5 V$
- ☐ $V_{OL} = 0 V$
- ☐ $V_{IL} = 1.1 V$
- ☐ $V_{IH} = 1.4 V$
- ☐ $N_{MH} = V_{OH} - V_{IH} = 1.1 V$
- ☐ $N_{ML} = V_{IL} - V_{OL} = 1.1 V$
- ☐ $V_M = 1.25 V$



Switch logic


Static Logic Gate

- At every point in time (except during the switching transients) each **gate output is connected to either V_{DD} or V_{SS}** via a low resistive path.
- The outputs of the gate **assumes at all times the value of the Boolean function** implemented by the circuit (ignoring, once again, the transient effects during switching periods).

Example: CMOS Inverter

Building logic from switches


Series

 

AND

$Y = X$ if A AND B

Parallel

 


OR

$Y = X$ if A OR B

(output undefined if condition not true)

Logic using inverting switches


Series

 

NOR

$$Y = X \text{ if } \overline{A} \text{ AND } \overline{B} \\ = \overline{A + B}$$

Parallel

 


NAND

$$Y = X \text{ if } \overline{A} \text{ OR } \overline{B} \\ = \overline{AB}$$

(output undefined if condition not true)

Static Complementary CMOS

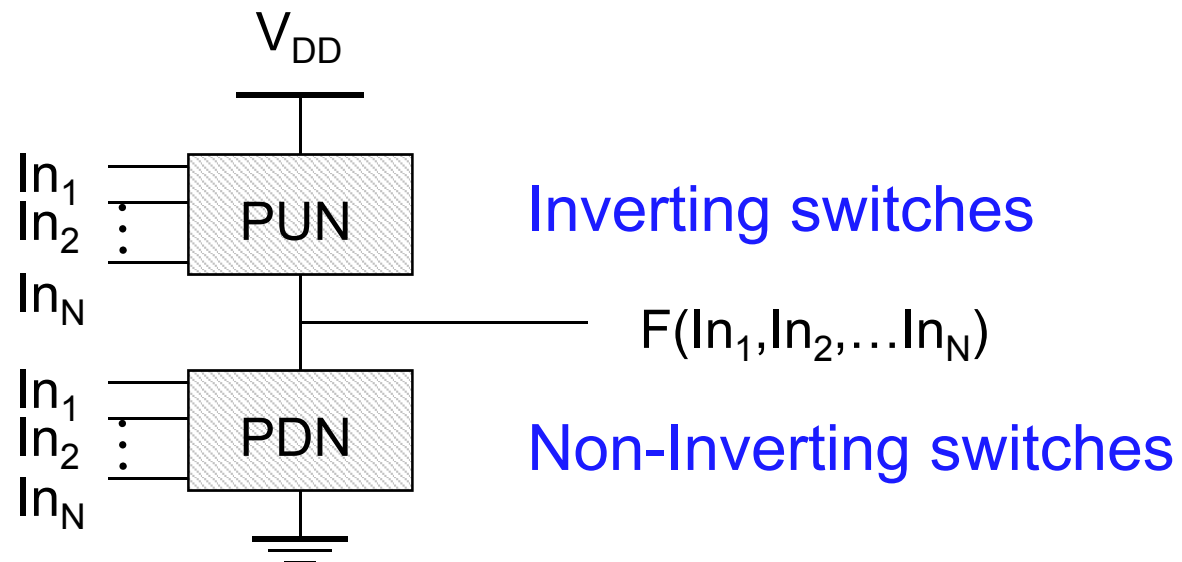

PUN and PDN are **dual** logic networks


PUN and PDN functions are **complementary**

Complementary CMOS Logic Style

- PUN is the **dual** to PDN
(can be shown using DeMorgan's Theorems)

$$\overline{A + B} = \overline{A} \overline{B}$$
$$\overline{AB} = \overline{A} + \overline{B}$$

- Static CMOS gates are always inverting

 


AND = NAND + INV

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


- PDN: $G = AB \Rightarrow$ Conduction to GND
- PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}
- $\overline{G(\text{In}_1, \text{In}_2, \text{In}_3, \dots)} \equiv F(\overline{\text{In}_1}, \overline{\text{In}_2}, \overline{\text{In}_3}, \dots)$

Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 


Complex CMOS Gate

$$\text{OUT} = \overline{D + A \cdot (B + C)}$$
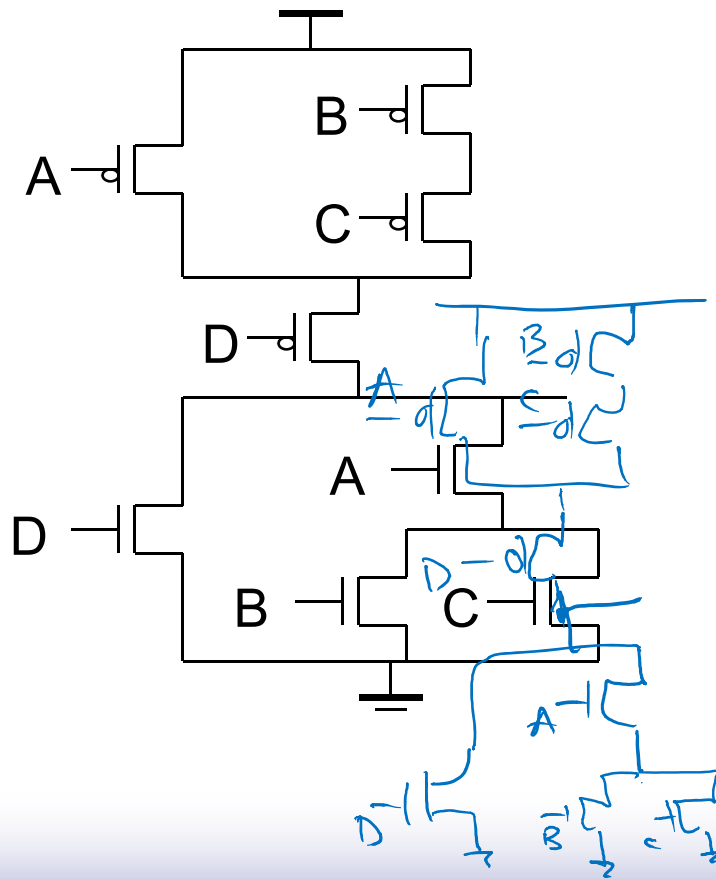
$$\text{OUT} = \overline{D \cdot A + B \cdot C}$$




Non-inverting logic

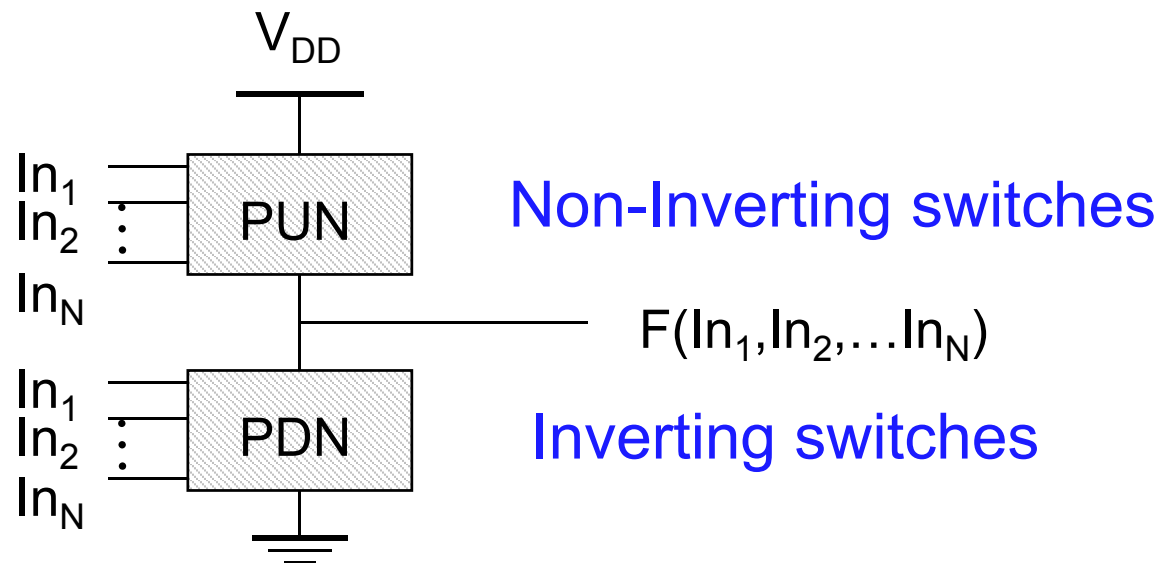

*Why is this
a bad idea?*

PUN and PDN are **dual** logic networks
PUN and PDN functions are **complementary**

Switch Limitations

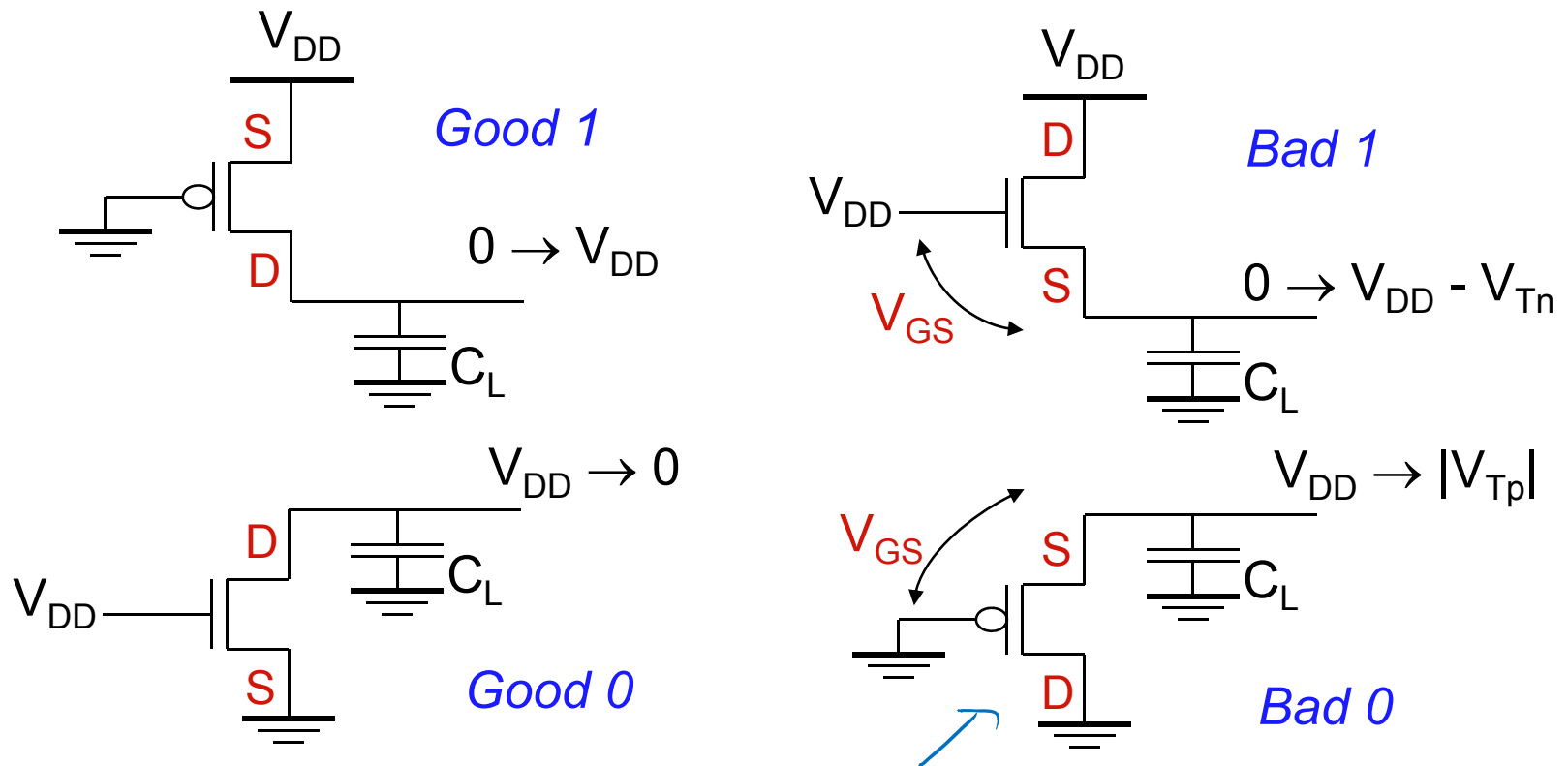


$$V_{OL} = |V_{Tp}|$$

$$V_{OH} = V_{DD} - V_{Tn}$$

Transmission Gate

 
- ❑ Transmission gates are the way to build “switches” in CMOS.
- ❑ In general, both transistor types are needed:
 - ❑ nFET to pass zeros.
 - ❑ pFET to pass ones.
- ❑ The transmission gate is bi-directional (unlike logic gates).





- ❑ Does not directly connect to V_{DD} and GND, but can be combined with logic gates or buffers to simplify many logic structures.

Transmission-gate Multiplexor

2-to-1 multiplexor:
 $C = sa + s'b$

 


Switches simplify the implementation:

  

Compare the cost to logic gate implementation.


4-to-1 Transmission-gate Mux

 

- ❑ The series connection of pass-transistors in each branch effectively forms the AND of $s1$ and $s0$ (or their complement).
- ❑ Compare cost to logic gate implementation

Alternative 4-to-1 Multiplexor

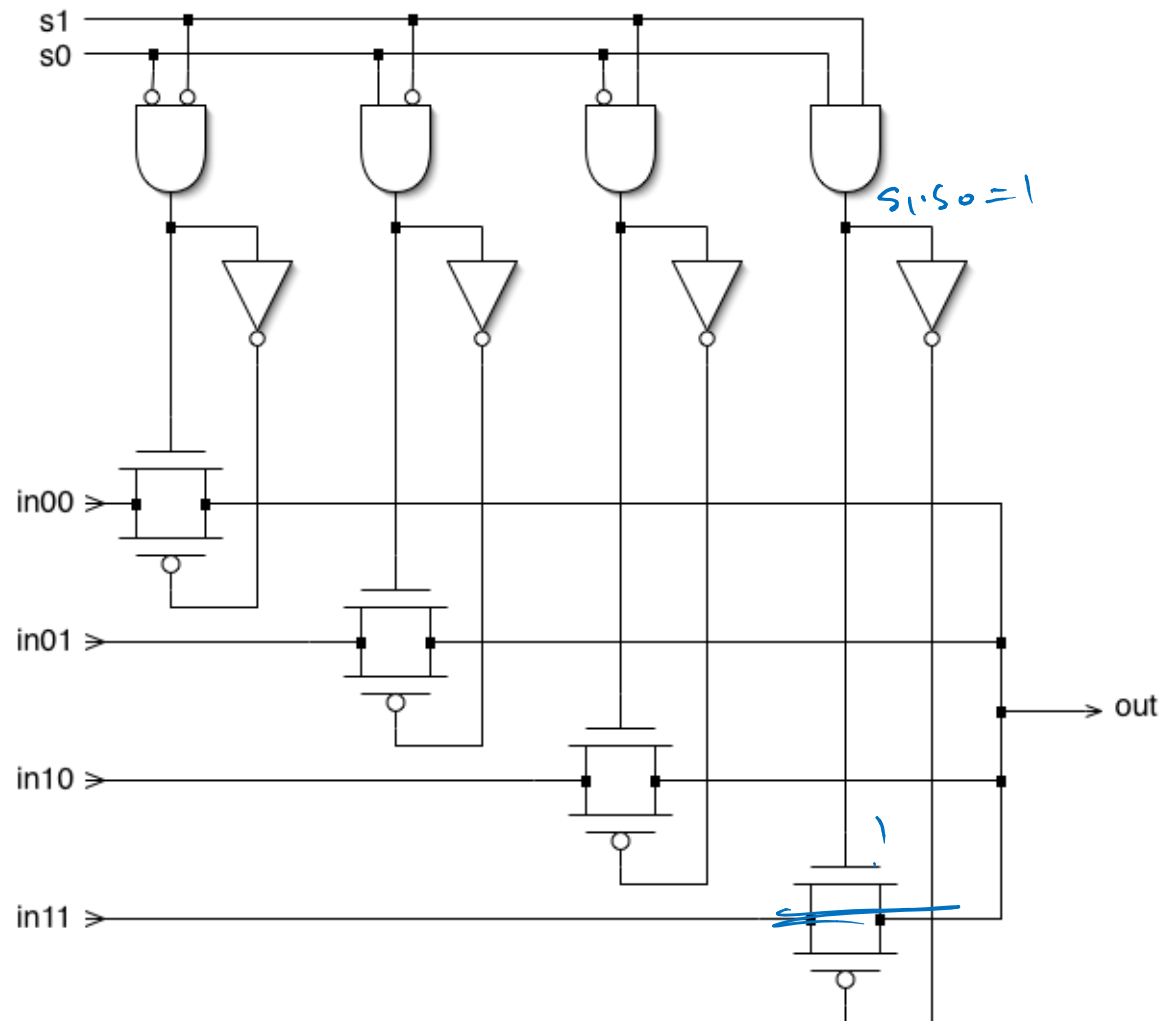- ❑ This version has less delay from in to out.
- ❑ In both versions, care must be taken to avoid turning on multiple paths simultaneously (shorting together the inputs).



Tri-state Buffers


Tri-state Buffer:



OE	IN	OUT
0	0	0
0	1	1
1	0	Z
1	1	Z


"high impedance"
(output disconnected)

Variations:

 


OE	IN	OUT
0	-	Z
1	0	1
1	1	0

Inverting buffer

 


OE	IN	OUT
0	0	0
0	1	1
1	-	Z

Inverted enable

 


 transmission
gate useful in
implementation




Tri-state Buffers

 Tri-state buffers enable "bidirectional" connections.



 
Tri-state buffers are used when multiple circuits all connect to a common wire. Only one circuit at a time is allowed to drive the bus. All others "disconnect" their outputs, but can "listen".






Tri-state Based Multiplexor

Transistor Circuit for inverting multiplexor:

Multiplexor

 


If $s=1$ then $c=a$

   

Summary:


Complimentary CMOS Properties

 - ❑ Full rail-to-rail swing
- ❑ Symmetrical VTC
- ❑ No static power dissipation
- ❑ Direct path current during switching




Transient properties


The Switch Revisited

 

The Switch Inverter: Transient Response

 

(a) Low-to-high

 


(b) High-to-low


$$t_{pHL} = f(R_{on}C_L) \\ = 0.69 R_n C_L$$

Switch Parasitic Model

The pull-down switch (NMOS)

 

Minimum-size switch

 


Sizing the transistor (factor W)


↑
Changing the width

Switch Parasitic Model


The pull-up switch (PMOS)

 

Minimum-size switch

 


Sized for symmetry

 

General sizing

Inverter Parasitic Model

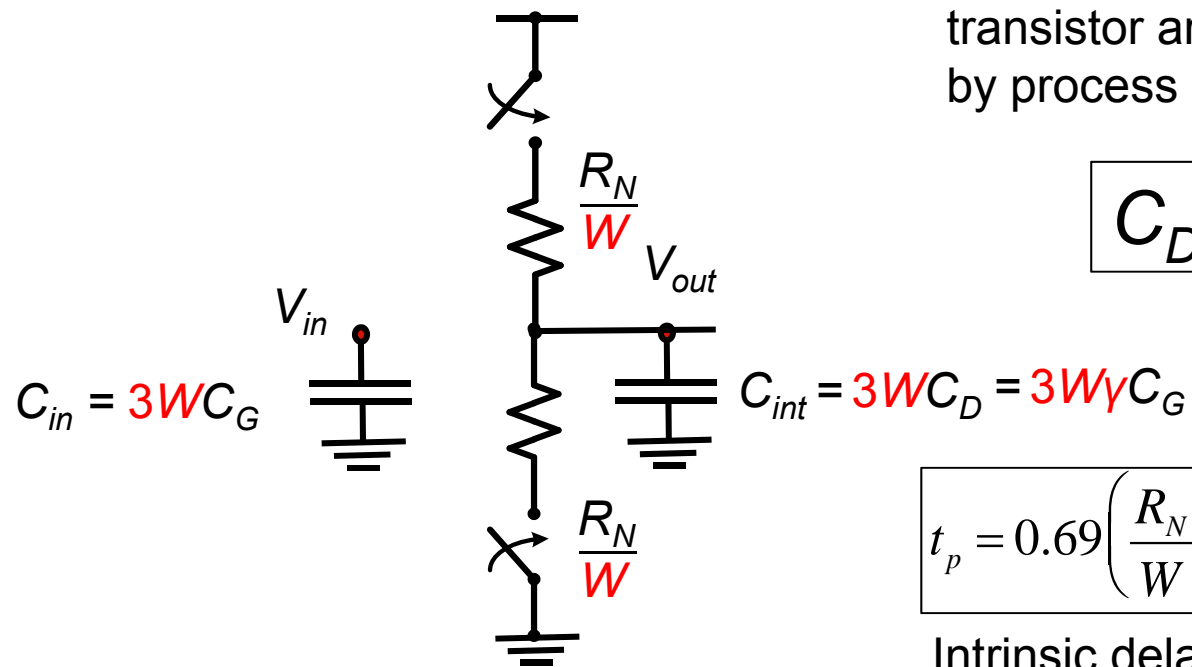


Drain and gate capacitance of transistor are **directly** related by process ($\gamma \approx 1$)

$$C_D = \gamma C_G$$

$$t_p = 0.69 \left(\frac{R_N}{W} \right) (3W\gamma C_G) = 0.69(3\gamma) R_N C_G$$

Intrinsic delay of inverter
independent of size

Inverter with Load Capacitance

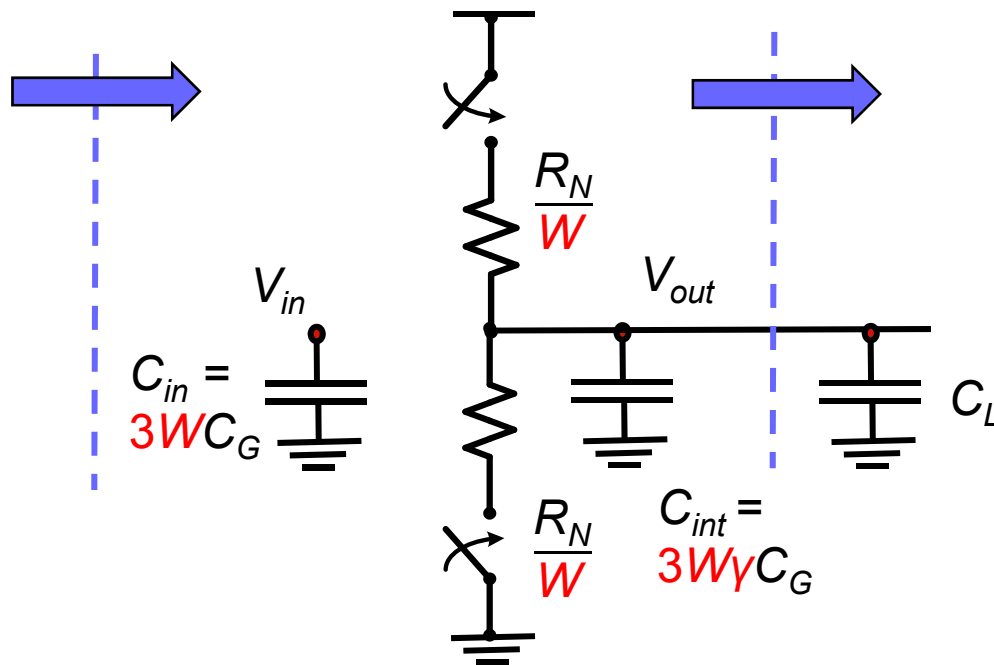

$$\begin{aligned}
 t_p &= 0.69 \left(\frac{R_N}{W} \right) (C_{int} + C_L) \\
 &= 0.69 \left(\frac{R_N}{W} \right) (3W\gamma C_G + C_L) \\
 &= 0.69 (3C_G R_N) \left(\gamma + \frac{C_L}{C_{in}} \right) \\
 &= t_{inv} \left(\gamma + \frac{C_L}{C_{in}} \right) = t_0 (\gamma + f)
 \end{aligned}$$


f = **fanout** = ratio between load and input capacitance of gate

Inverter Delay Model

$$t_p = t_{inv}(\gamma + f)$$

t_{inv} technology constant

 - Can be dropped from expression
- Delay unit-less variable (expressed in unit delays)



Question: how does transistor sizing (W) impact delay?