

Homework 10

Kevin Chau
23816929
CS150bcd


1. Primitive Polynomials:

5 bit: $x^5 + x^2 + 1$



7 bit: $x^7 + x^3 + 1$

$sel = 0 \rightarrow 5 \text{ bit}$

$sel = 1 \rightarrow 7 \text{ bit}$

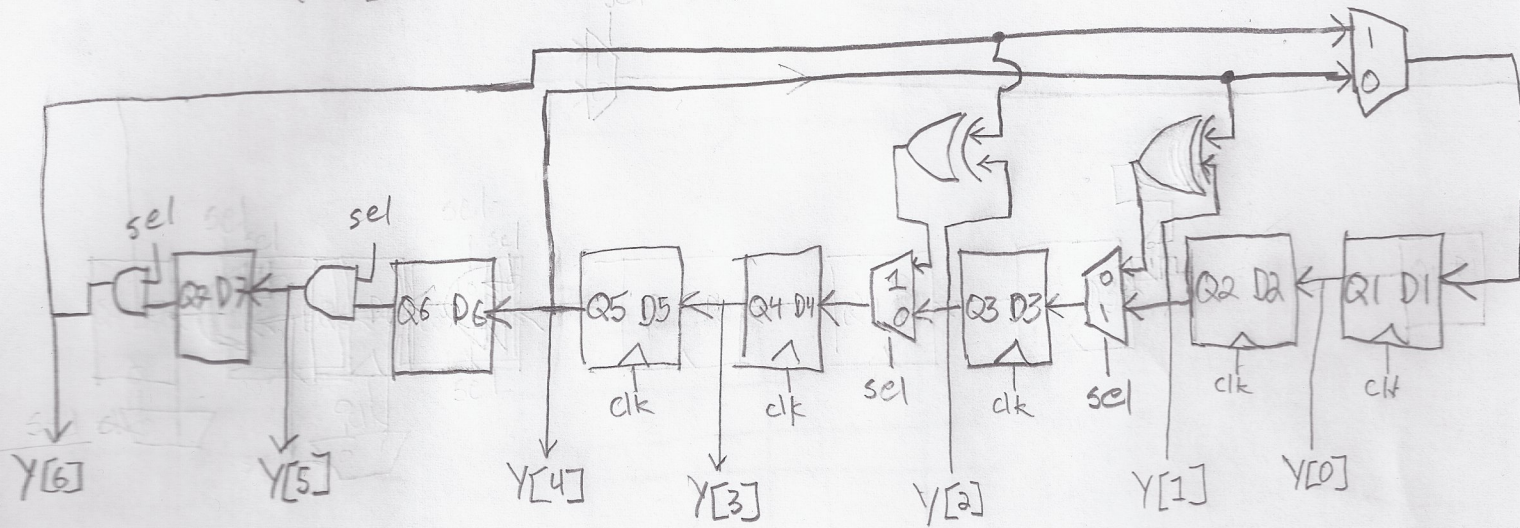
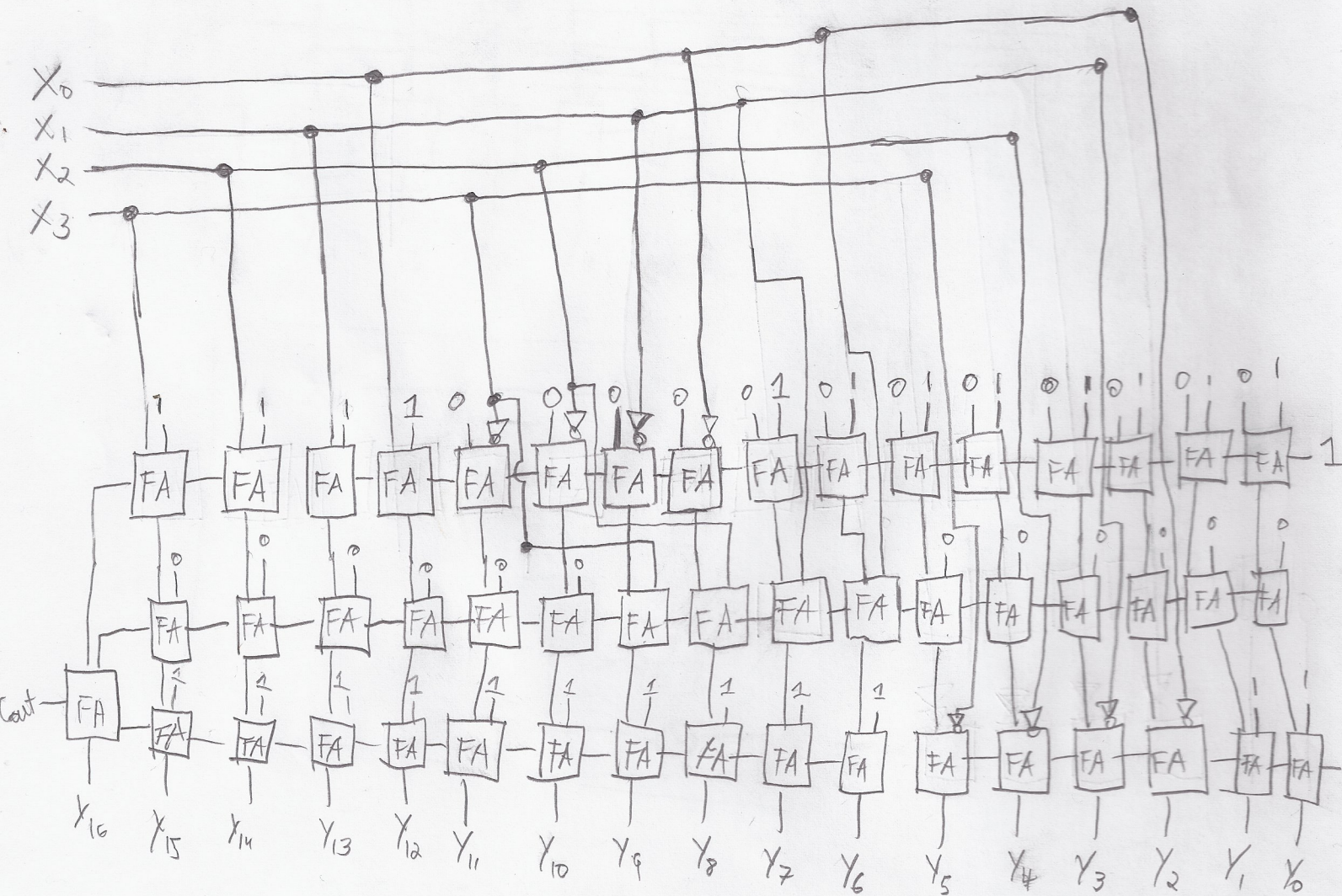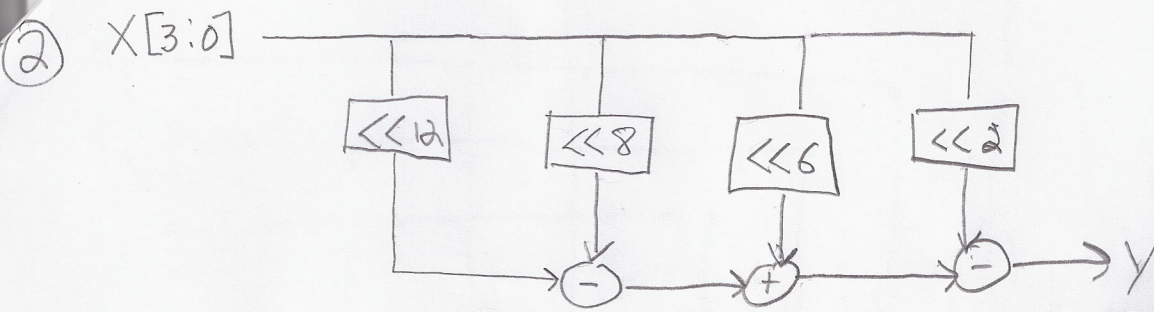
$$3900_{10} = F3C_{16} = 0b111100111100 = 1000T01000T00 = 2^{12} - 2^8 + 2^6 - 2^2$$






49 Full Adders

We can reduce the number of Adders by noticing

$$\text{that } 2^{12} - 2^8 + 2^6 - 2^2 = [2^6 - 2^2]2^6 + [2^6 - 2^2]$$

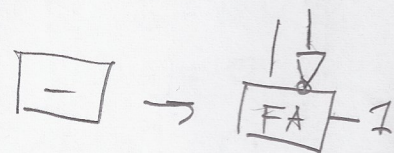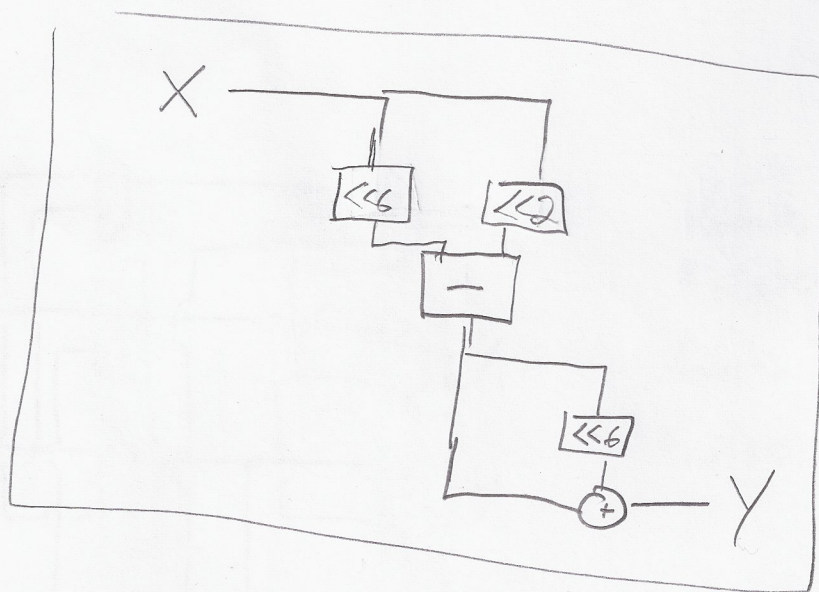
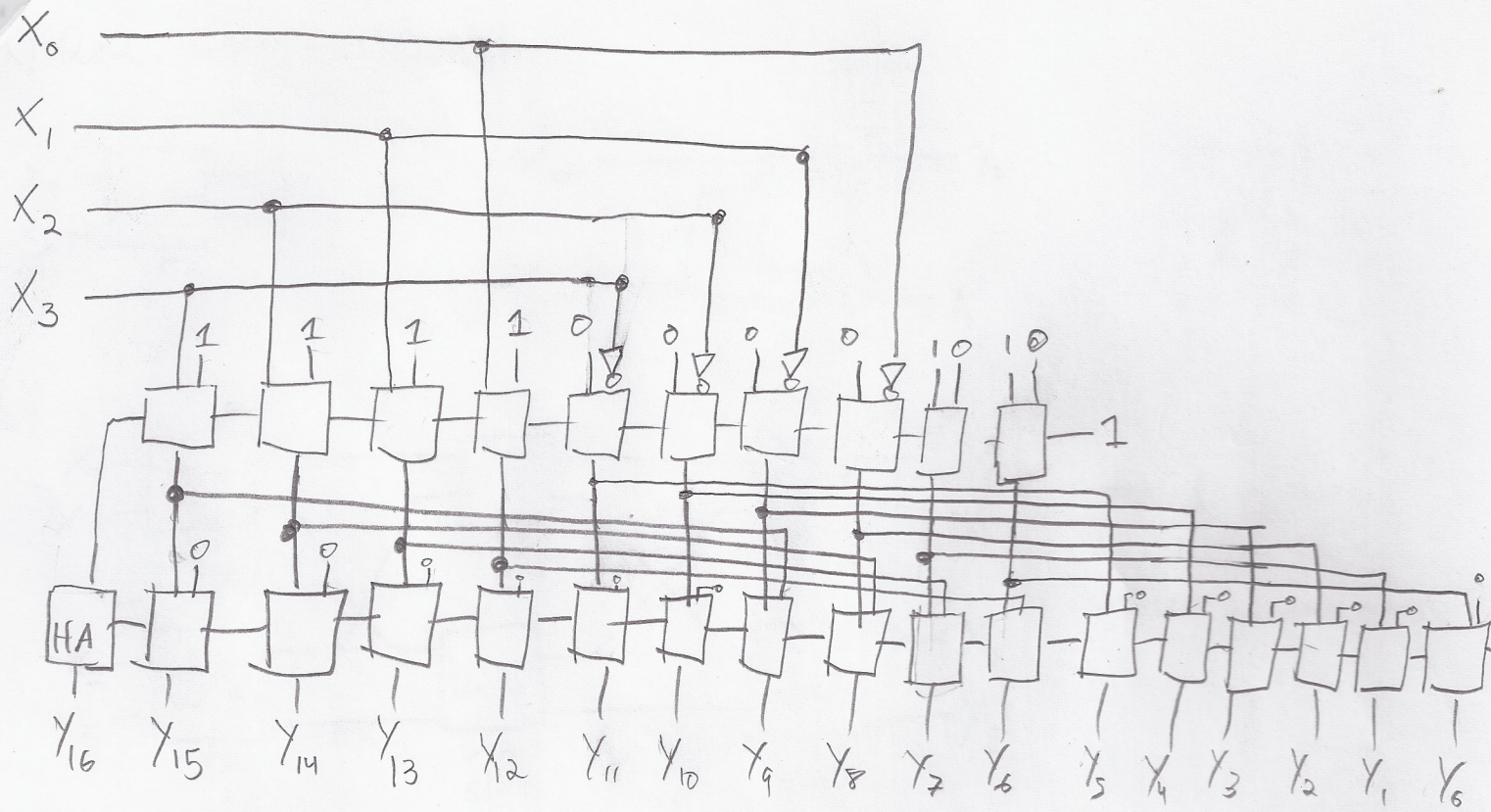
so that we just need 1 subtraction stage and we simply add that result to a shifted by 6 result for stage 2.



26 Full Adders


(3)

a) 2x2 Cross Bar Switch

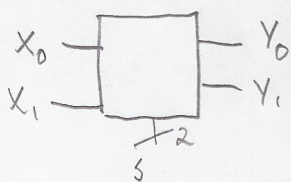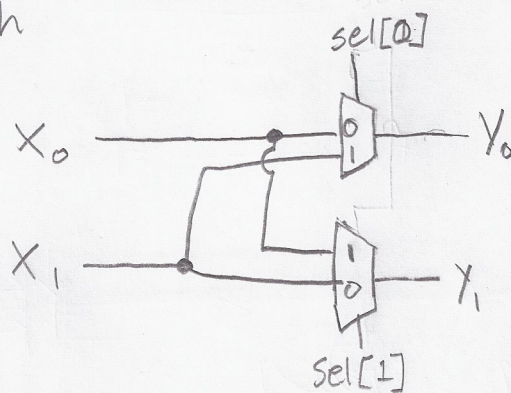 \Rightarrow 


sel	Y_0	Y_1
00	X_0	X_0
10	X_0	X_1
01	X_1	X_1
11	X_1	X_0

b)

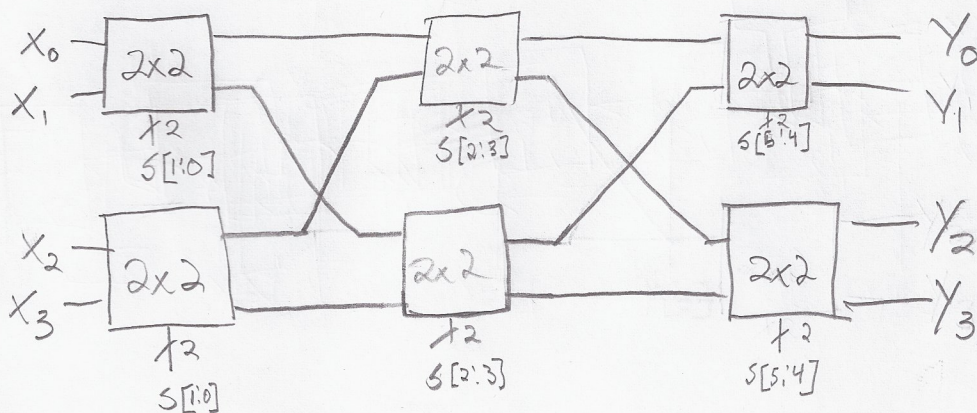

Need a
controller to
select permutations

4.

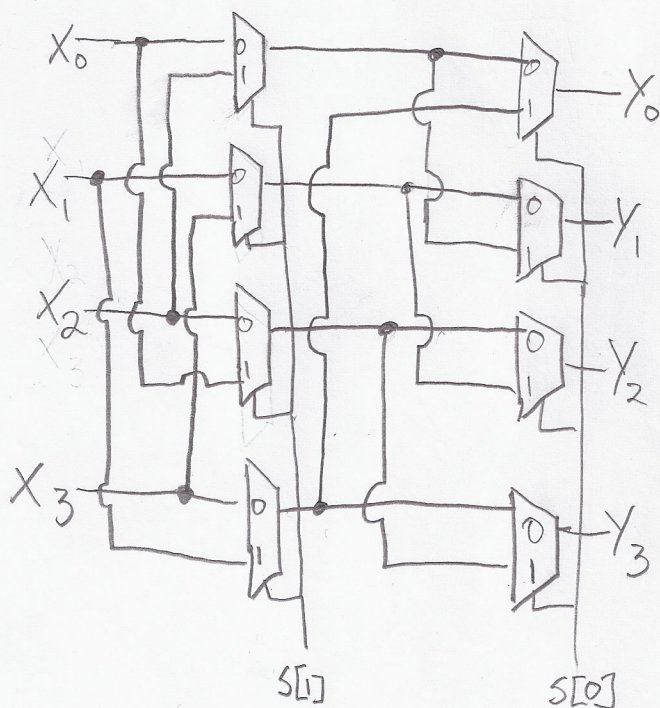

Rotate 0: $S[1:0] = 00$
 Rotate 2: $S[1:0] = 10$
 Rotate 1: $S[1:0] = 01$
 Rotate 3: $S[1:0] = 11$