



CS150 Discussion 1

Simon Scott

Discussion Structure

- Material not covered in lecture
- FPGA-specific material
- Problems relating to homework
- Questions
- ???

Past FPGA Projects

- Software-defined radio using Ettus Logic USRP
- RHINO: FPGA board for radar and astronomy research



VEGAS: spectrometer for
Greenbank Observatory (100Gbps!)

- Office hours: Thursdays 1-2pm, Cory 125



ASIC vs FPGA


ASIC	FPGA
Long time to fabricate	Immediate results
Only debug in simulation	Debug on dev. boards
Fired if make mistake	Bugs easily fixed
Maximum performance	Lower performance, but can use multiple in parallel
Most jobs at established companies	Many startup jobs

- Good choice 😊



FPGAs



CS150 Project platform: Xilinx ML505-110

 

FPGA: Xilinx Virtex-5 XC5VLX110T








Virtex-5 “die photo”

  

A die is an unpackaged part


From die to PC board ...

Ball Grid
Array
(BGA)
Flip-Chip
Package

     

FPGA Overview

 - ❑ Basic idea: two-dimensional array of logic blocks and flip-flops with a means for the user to configure (program):
 1. the interconnection between the logic blocks,
 2. the function of each block.



Simplified version of FPGA internal architecture:

Why are FPGAs Interesting?

□ Technical viewpoint:

- For hardware/system-designers, like ASICs only better! “Tape-out” new design every few minutes/hours.
- Does the “reconfigurability” or “reprogrammability” offer other advantages over fixed logic?
 - Dynamic reconfiguration? In-field reprogramming? Self-modifying hardware, evolvable hardware?

Why are FPGAs Interesting?


- ❑ Staggering logic capacity growth (10000x):

Year Introduced	Device	Logic Cells	“logic gate equivalents”
1985	XC2064	128	1024
2011	XC7V2000T	1,954,560	15,636,480

- FPGAs have tracked Moore’s Law better than any other programmable device.


Why are FPGAs Interesting?

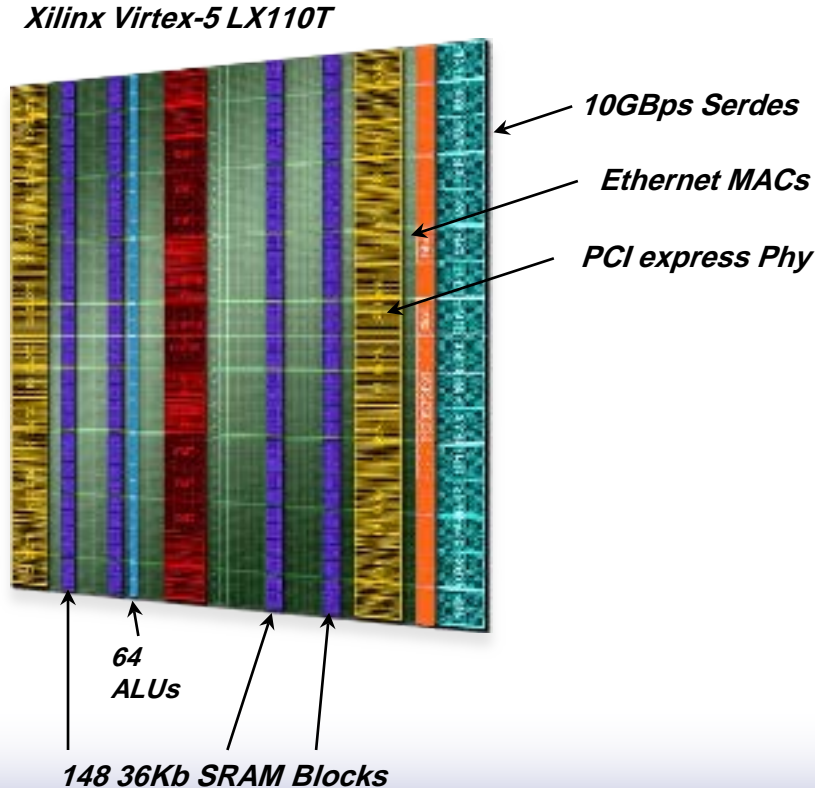- Logic capacity now only part of the story: on-chip RAM, high-speed I/Os, “hard” function blocks, ...
- Modern FPGAs are “reconfigurable systems”




FPGAs are in widespread use

 Far more designs are implemented in FPGA than in custom chips.



User Programmability

- *Latch-based (Xilinx, Altera, ...)*

 

- + *reconfigurable*
- *volatile*
- *relatively large*


- ❑ Latches are used to:

1. control a switch to make or break cross-point connections in the interconnect
2. define the function of the logic blocks
3. set user options:
 - within the logic blocks
 - in the input/output blocks
 - global reset/clock

- ❑ “Configuration bit stream” is loaded under user control


Background (review) for upcoming

 - A MUX or multiplexor is a combinational logic circuit that chooses between 2^N inputs under the control of N control signals.




- A latch is a 1-bit memory (similar to a flip-flop).

Idealized FPGA Logic Block

 

- ❑ 4-input look up table (LUT)
 - implements combinational logic functions
- ❑ Register
 - optionally stores output of LUT

4-LUT Implementation

 

□ n-bit LUT is implemented as a $2^n \times 1$ memory:

- inputs choose one of 2^n memory locations.
- memory locations (latches) are normally loaded with values from user's configuration bit stream.
- Inputs to mux control are the CLB inputs.

□ Result is a general purpose "logic gate".

- n-LUT can implement any function of n inputs!

LUT as general logic gate

- An n-lut as a direct implementation of a function truth-table.
- Each latch location holds the value of the function corresponding to one input combination.

Example: 2-lut

INPUTS	AND	OR	
00	0	0	
01	0	1	
10	0	1	• • •
11	1	1	

Implements any function of 2 inputs.


How many of these are there?

How many functions of n inputs?

Example: 4-lut

INPUTS		
0000	F(0,0,0,0)	← store in 1st latch
0001	F(0,0,0,1)	← store in 2nd latch
0010	F(0,0,1,0)	←
0011	F(0,0,1,1)	←
0011		
0100	•	
0101	•	
0110	•	
0111		
1000		
1001		
1010		
1011		
1100		
1101		
1110		
1111		


FPGA Generic Design Flow

 

- **Design Entry:**
 - Create your design files using:
 - schematic editor or
 - HDL (hardware description languages: Verilog, VHDL)
- **Design Implementation:**
 - Logic synthesis (in case of using HDL entry) followed by,
 - Partition, place, and route to create configuration bit-stream file
- **Design verification:**
 - Optionally use simulator to check function,
 - Load design onto FPGA device (cable connects PC to development board), optional “logic scope” on FPGA
 - check operation at full speed in real environment.


Example Partition, Placement, and Route

- *Idealized FPGA structure:*

 

□ Example Circuit:

- collection of gates and flip-flops

 

Circuit combinational logic must be “covered” by 4-input 1-output LUTs.


Flip-flops from circuit must map to FPGA flip-flops.

(Best to preserve “closeness” to CL to minimize wiring.)

Best placement in general attempts to minimize wiring.


Vdd, GND, clock, and global resets are all “prewired”.

Example Partition, Placement, and Route

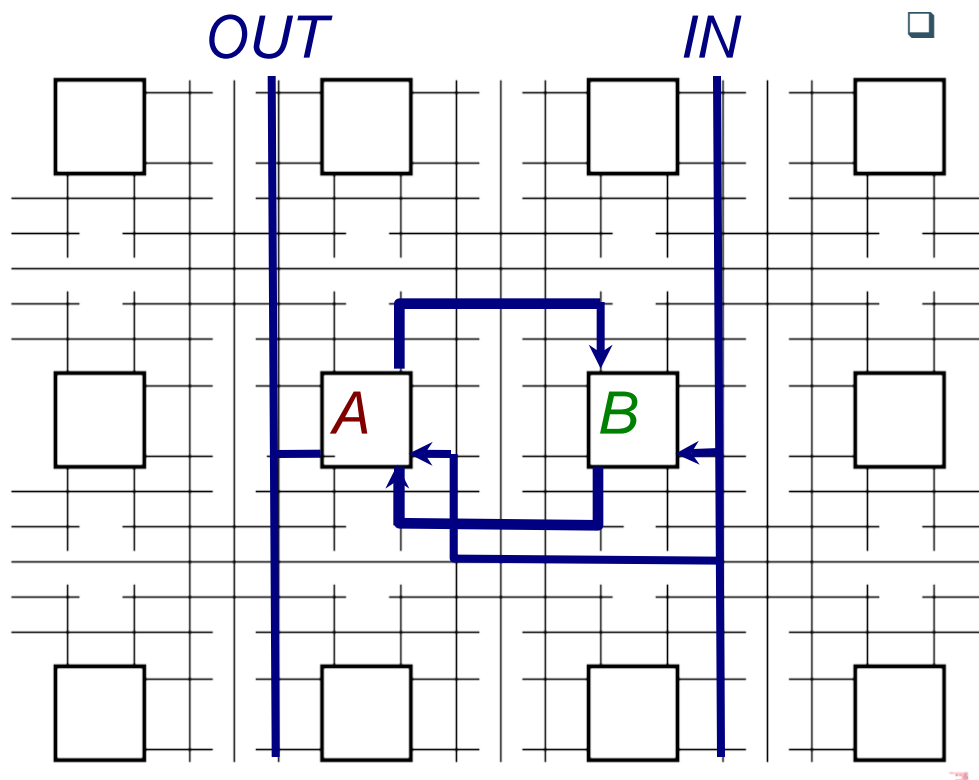

Example Circuit:

- collection of gates and flip-flops

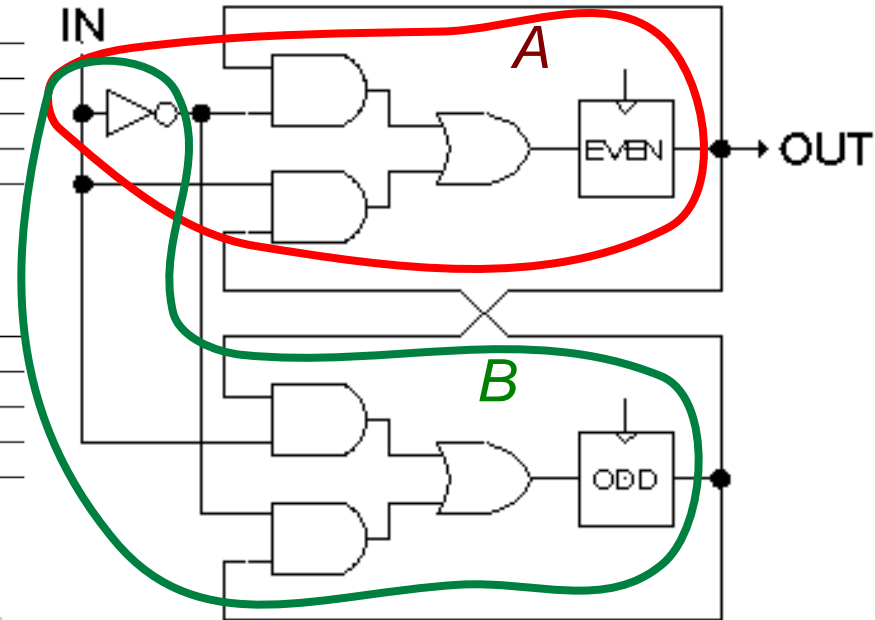

Two partitions. Each has single output, no more than 4 inputs, and no more than 1 flip-flop. In this case, inverter goes in both partitions.

Note: the partition can be arbitrarily large as long as it has not more than 4 inputs and 1 output, and no more than 1 flip-flop.

*Colors represent
different types
of resources:*

Logic

Block RAM


DSP (ALUs)

Clocking

I/O


Serial I/O + PCI

 *A routing fabric
runs throughout
the chip to wire
everything
together.*



Configurable Logic Blocks (CLBs)

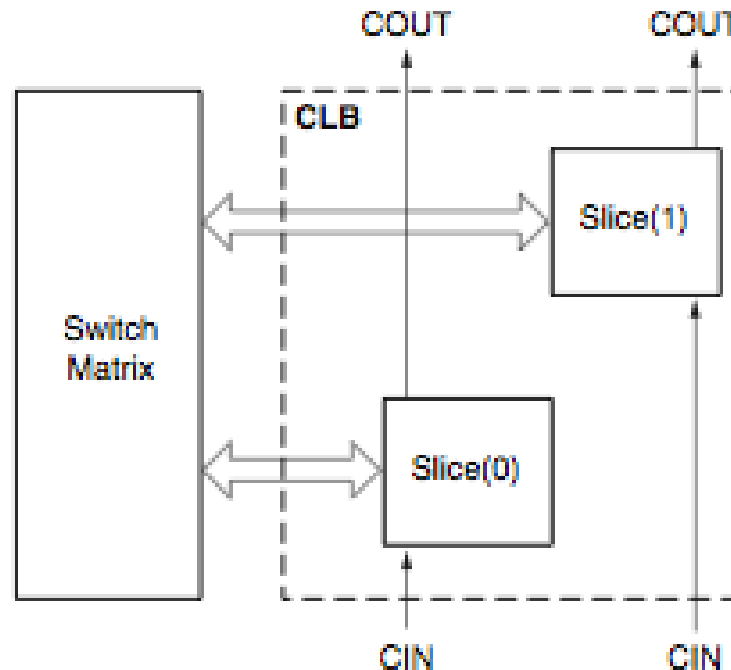Slices define regular connections to the switching fabric, and to slices in CLBs above and below it on the die.




The LX110T has 17,280 slices.

X-Y naming convention for slices

X0, X2, ... are lower CLB slices.

X1, X3, ... are upper CLB slices.


Y0, Y1, ... are CLB column positions.

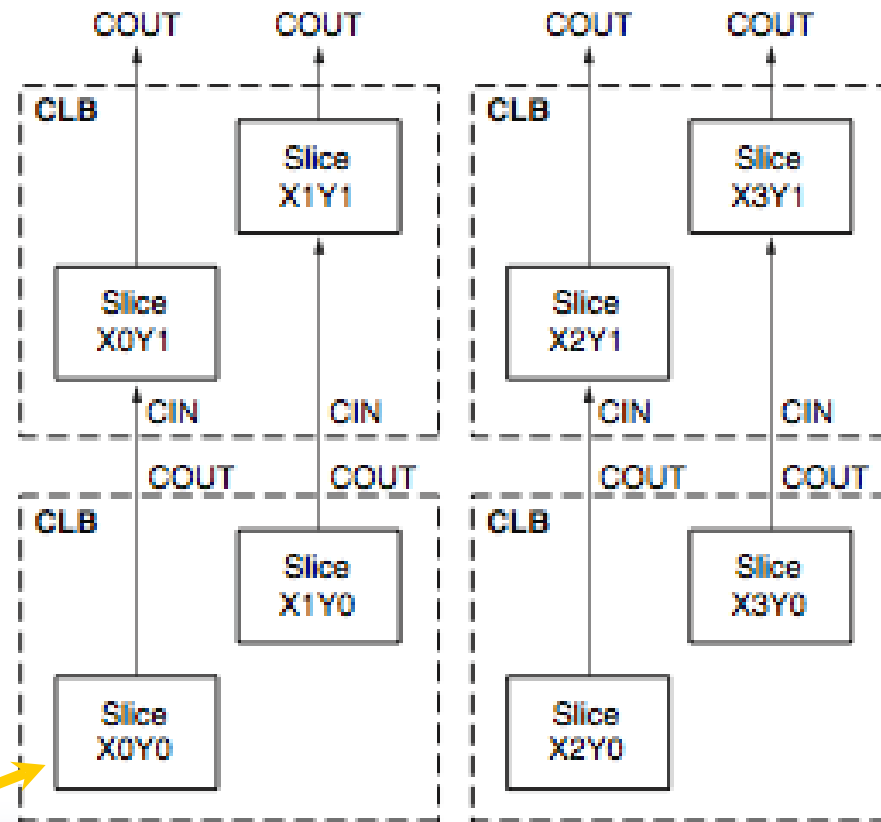


Lower-left corner of the die.

UQ190_5_02_122625

Atoms: 5-input Look Up Tables (LUTs)

 

$A[6:2]$	D
00000	1
00001	0
00010	1

 

Computes any 5-input logic function.

Timing is independent of function.

Latches set during configuration.

Virtex-5 6-LUTs: Composition of 5-LUTs

May be used
as one
6-input LUT
(D6 out) ...

... or as two
5-input LUTS
(D6 and D5)

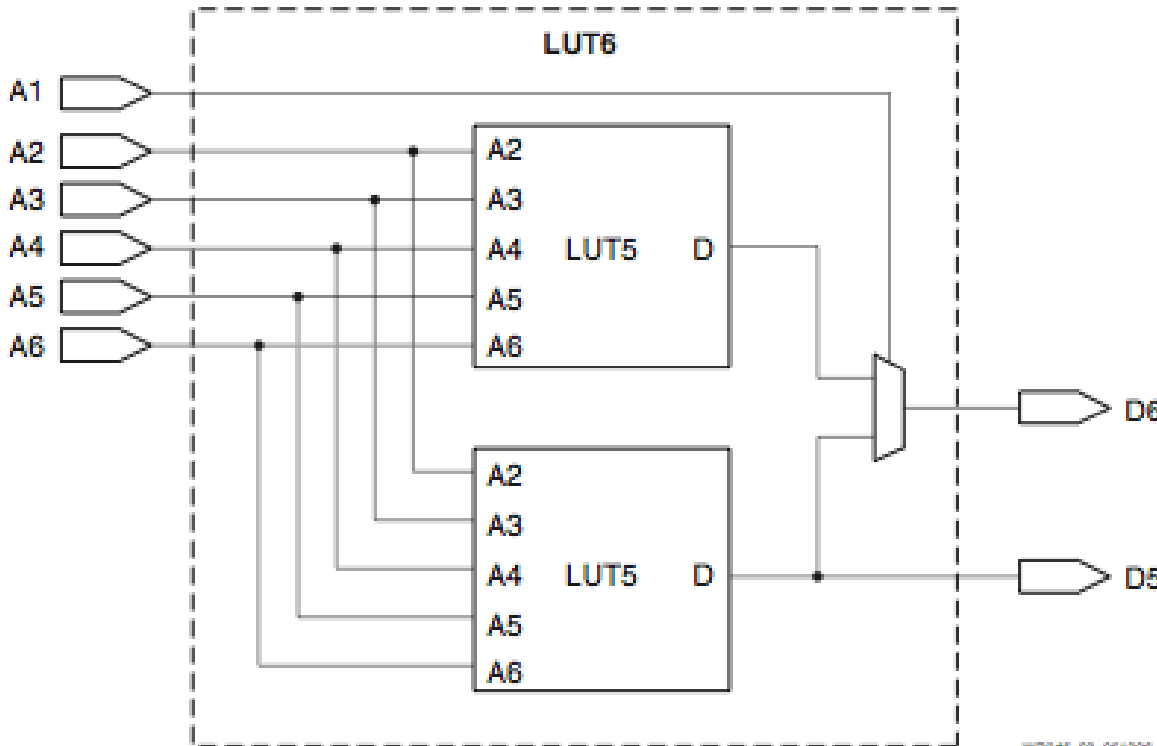



Figure 3: Block Diagram of a Virtex-5 6-Input LUT

The LX110T has 69,120 6-LUTs
6-LUT delay is 0.9 ns

*Combinational
logic*

(post configuration)

The simplest view of a slice

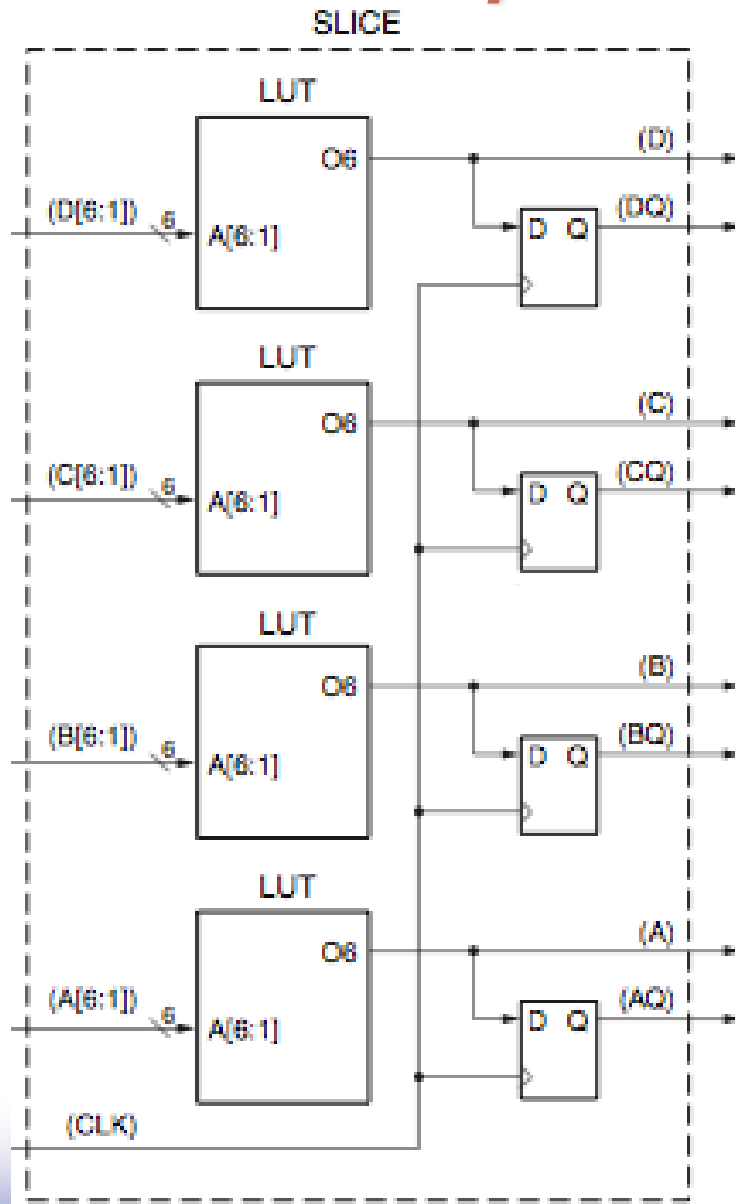


Four 6-LUTs

Four Flip-Flops

*Switching fabric may see
combinational and registered
outputs.*


*An actual Virtex-5 slice adds
many small features to this
simplified diagram. We show
them one by one ...*

Two 7-LUTs per slice ...

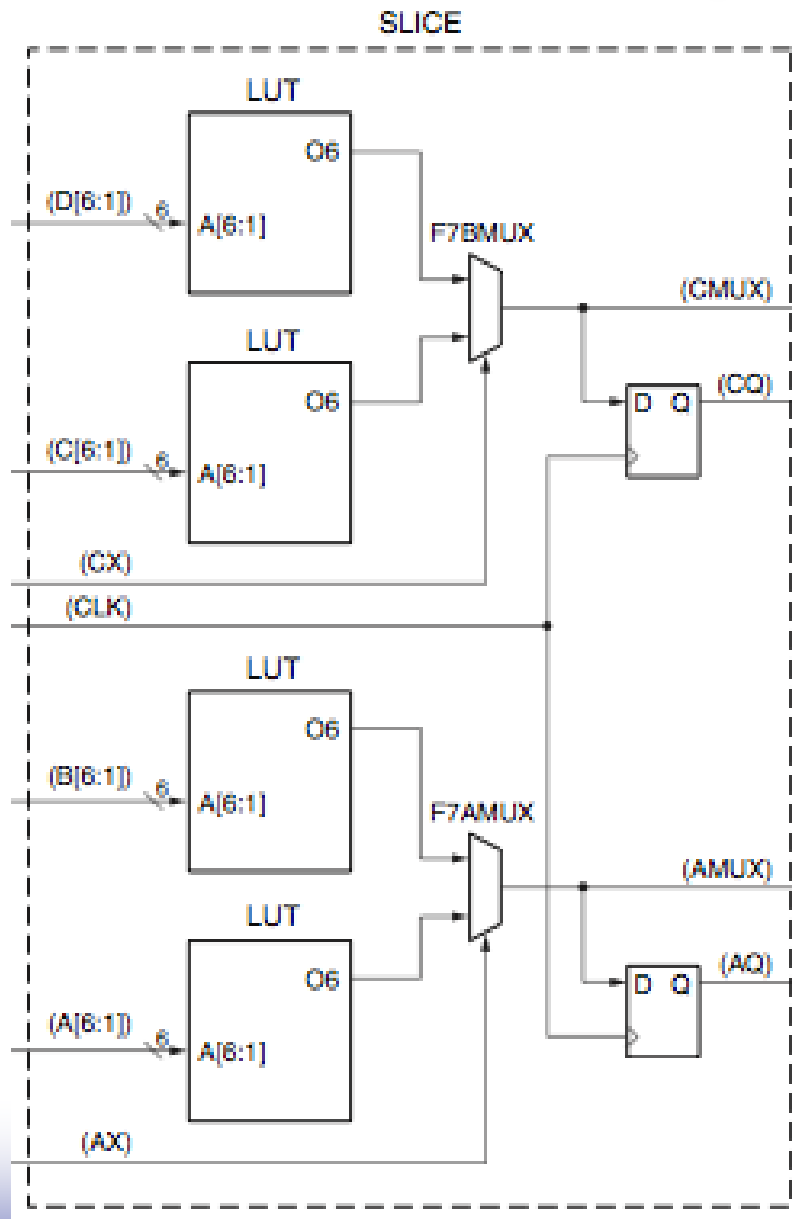

*Extra
multiplexers(F7AMUX,
F7BMUX)
Extra inputs
(AX and CX)*

Or one 8-LUTs per slice ...

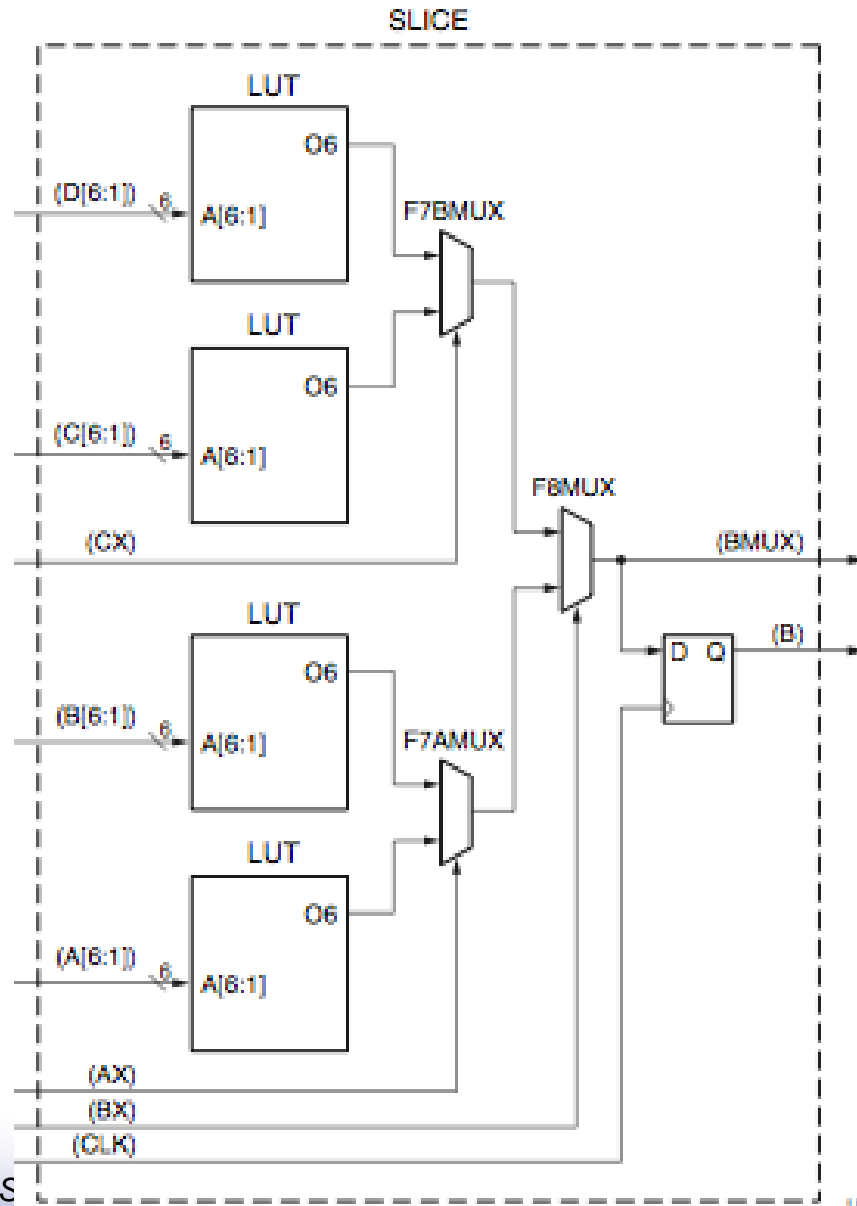


*Third
multiplexer(F8MUX)*

*Third input
(BX)*

*Configuring the
“n” of an n-LUT...*

Extra muxes to chose LUT option ...

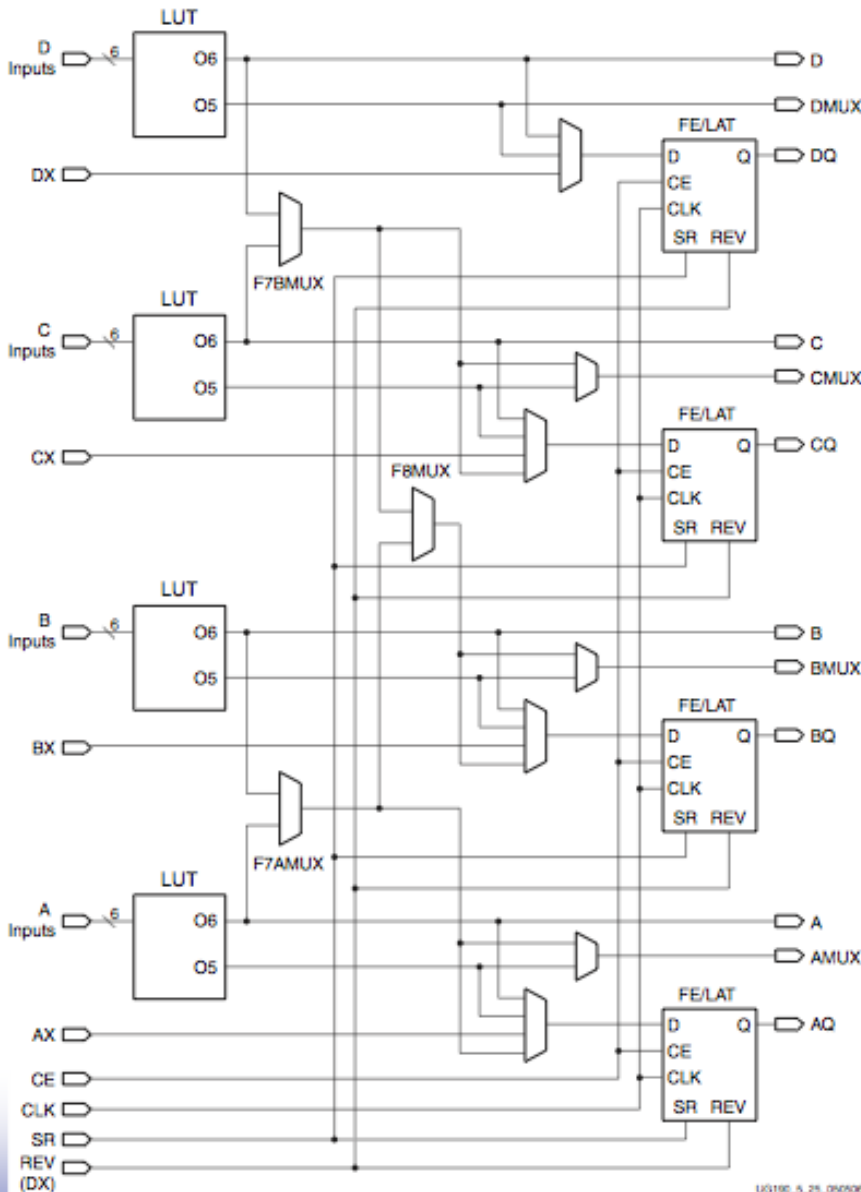


*From eight 5-LUTs
... to one 8-LUT.*

*Combinational
or registered outs.*


*Flip-flops unused by
LUTs can be used
standalone.*

Virtex 5 Vertical Logic

 We can map ripple-carry addition onto carry-chain block.



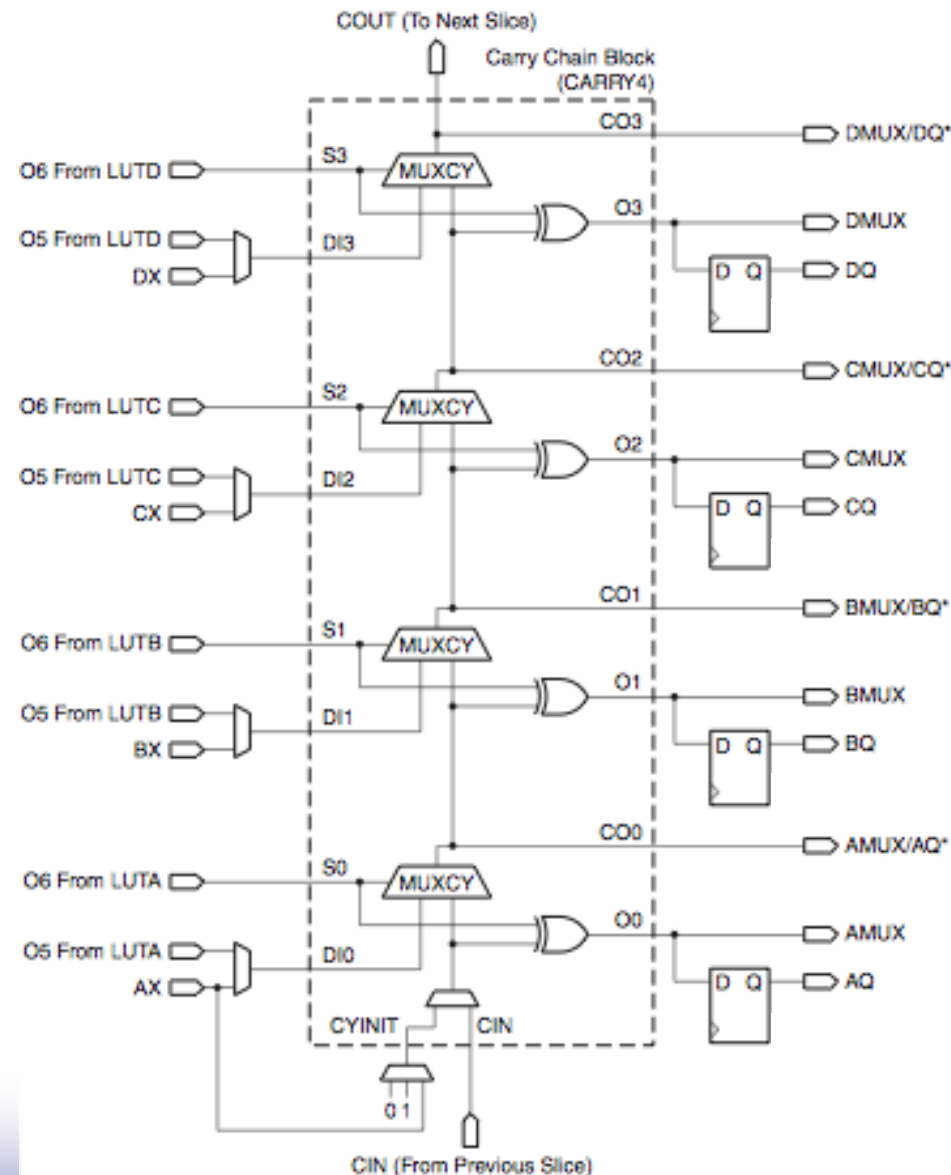The carry-chain block also useful for speeding up other adder structures and counters.




Putting it all together ... a SLICEL.


The previous slides explain all SLICEL features.

About 50% of the 17,280 slices in an LX110T are SLICELs.

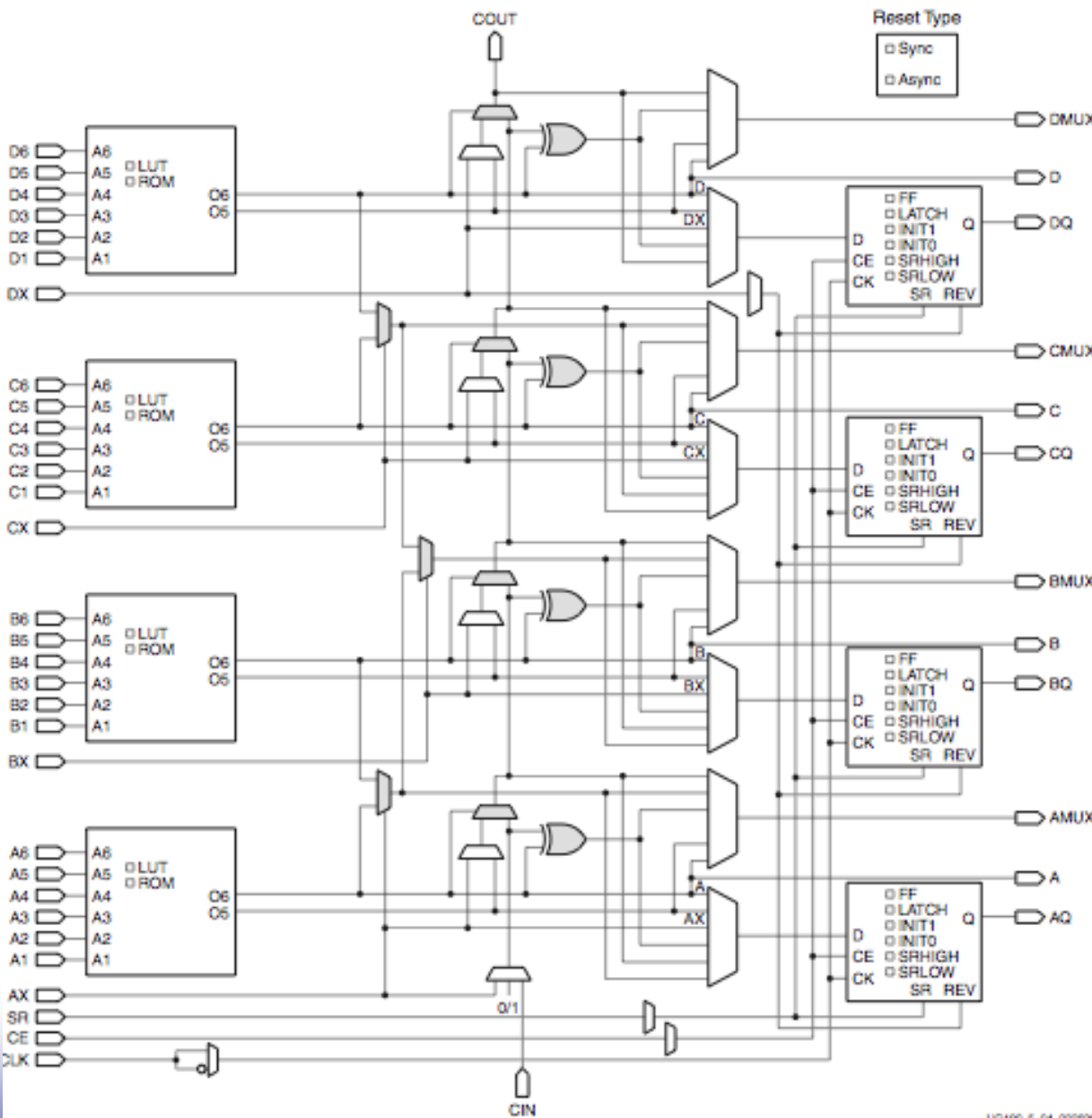The other slices are SLICEMs, and have extra features.



Recall: 5-LUT architecture ...

 


$A[6:2]$ D

00000
00001
00010

1
0
1

11101
11110
11111

0
0
1

 


32 Latches.

Configured to 1 or 0.

Some parts of a logic design need many state elements.

SLICEMs replace normal 5-LUTs with circuits that can act like 5-LUTs, but can alternatively use the 32 latches as RAM, ROM, shift registers.

Virtex-5 DSP48E Slice

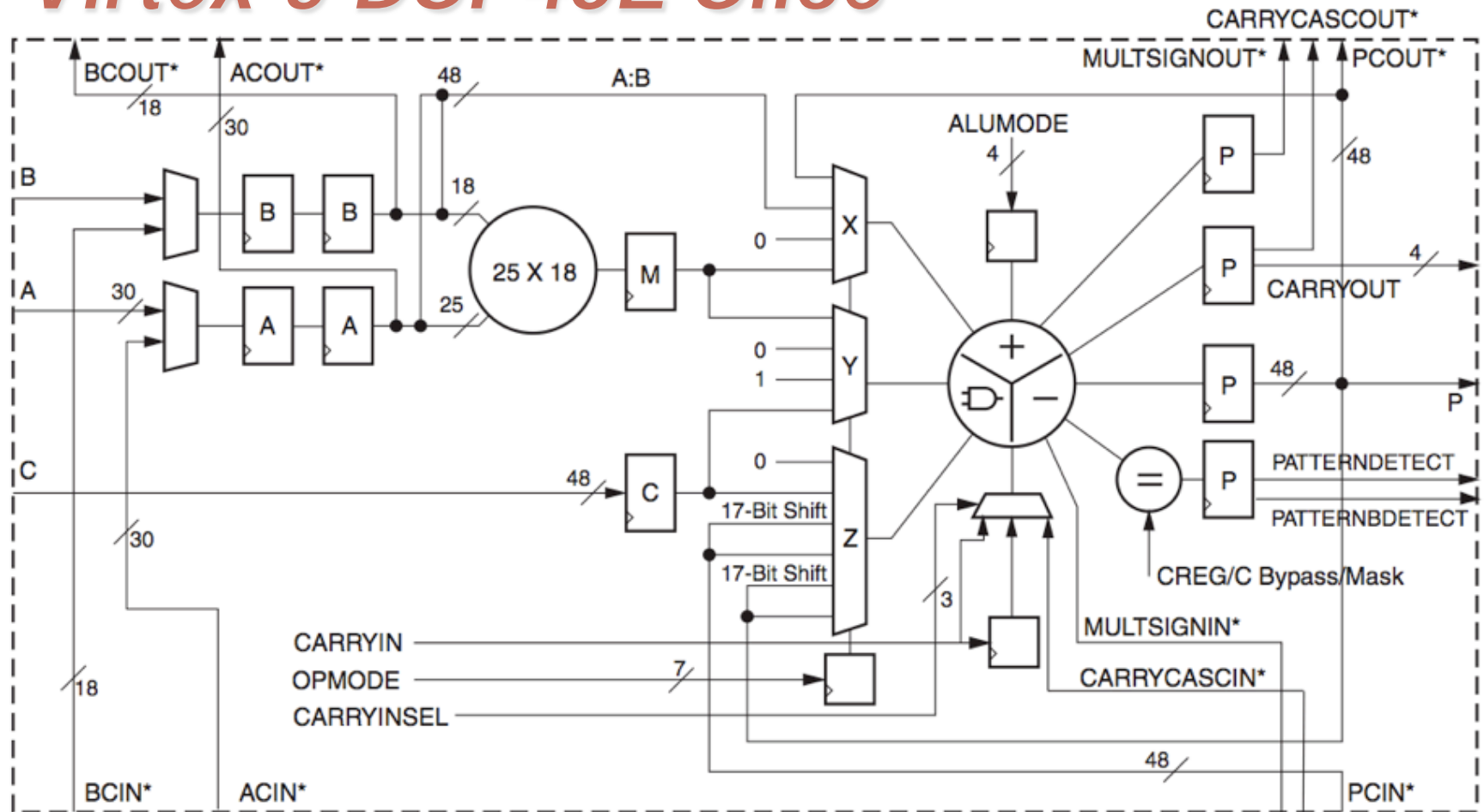

*These signals are dedicated routing paths internal to the DSP48E column. They are not accessible via fabric routing resources.

Efficient implementation of multiply, add, bit-wise logical.

LX110T has 64 in a single column.

UG182_c1_01_032806

Table 1: Virtex-5 FPGA Family Members

Device	Configurable Logic Blocks (CLBs)				Block RAM Blocks			CMTs ⁽⁴⁾	PowerPC Processor Blocks	Endpoint Blocks for PCI Express	Ethernet MACs ⁽⁵⁾	Max RocketIO Transceivers ⁽⁶⁾		Total I/O Banks ⁽⁸⁾	Max User I/O ⁽⁷⁾
	Array (Row x Col)	Virtex-5 Slices ⁽¹⁾	Max Distributed RAM (Kb)	DSP48E Slices ⁽²⁾	18 Kb ⁽³⁾	36 Kb	Max (Kb)					GTP	GTX		
XC5VLX30	80 x 30	4,800	320	32	64	32	1,152	2	N/A	N/A	N/A	N/A	N/A	13	400
XC5VLX50	120 x 30	7,200	480	48	96	48	1,728	6	N/A	N/A	N/A	N/A	N/A	17	560
XC5VLX85	120 x 54	12,960	840	48	192	96	3,456	6	N/A	N/A	N/A	N/A	N/A	17	560
XC5VLX110	160 x 54	17,280	1,120	64	256	128	4,608	6	N/A	N/A	N/A	N/A	N/A	23	800
XC5VLX155	160 x 76	24,320	1,640	128	384	192	6,912	6	N/A	N/A	N/A	N/A	N/A	23	800
XC5VLX220	160 x 108	34,560	2,280	128	384	192	6,912	6	N/A	N/A	N/A	N/A	N/A	23	800
XC5VLX330	240 x 108	51,840	3,420	192	576	288	10,368	6	N/A	N/A	N/A	N/A	N/A	33	1,200
XC5VLX20T	60 x 26	3,120	210	24	52	26	936	1	N/A	1	2	4	N/A	7	172
XC5VLX30T	80 x 30	4,800	320	32	72	36	1,296	2	N/A	1	4	8	N/A	12	360
XC5VLX50T	120 x 30	7,200	480	48	120	60	2,160	6	N/A	1	4	12	N/A	15	480
XC5VLX85T	120 x 54	12,960	840	48	216	108	3,888	6	N/A	1	4	12	N/A	15	480
XC5VLX110T	160 x 54	17,280	1,120	64	296	148	5,328	6	N/A	1	4	16	N/A	20	680
XC5VLX155T	160 x 76	24,320	1,640	128	424	212	7,632	6	N/A	1	4	16	N/A	20	680
XC5VLX220T	160 x 108	34,560	2,280	128	424	212	7,632	6	N/A	1	4	16	N/A	20	680
XC5VLX330T	240 x 108	51,840	3,420	192	648	324	11,664	6	N/A	1	4	24	N/A	27	960
XC5VSX35T	80 x 34	5,440	520	192	168	84	3,024	2	N/A	1	4	8	N/A	12	360
XC5VSX50T	120 x 34	8,160	780	288	264	132	4,752	6	N/A	1	4	12	N/A	15	480
XC5VSX95T	160 x 46	14,720	1,520	640	488	244	8,784	6	N/A	1	4	16	N/A	19	640
XC5VSX240T	240 x 78	37,440	4,200	1,056	1,032	516	18,576	6	N/A	1	4	24	N/A	27	960
XC5VTX150T	200 x 58	23,200	1,500	80	456	228	8,208	6	N/A	1	4	N/A	40	20	680
XC5VTX240T	240 x 78	37,440	2,400	96	648	324	11,664	6	N/A	1	4	N/A	48	20	680
XC5VFX30T	80 x 38	5,120	380	64	136	68	2,448	2	1	1	4	N/A	8	12	360
XC5VFX70T	160 x 38	11,200	820	128	296	148	5,328	6	1	3	4	N/A	16	19	640
XC5VFX100T	160 x 56	16,000	1,240	256	456	228	8,208	6	2	3	4	N/A	16	20	680
XC5VFX130T	200 x 56	20,480	1,580	320	596	298	10,728	6	2	3	6	N/A	20	24	840
XC5VFX200T	240 x 68	30,720	2,280	384	912	456	16,416	6	2	4	8	N/A	24	27	960

Verilog

- Describes **hardware** NOT software
- Example:
 - $a = b + c$
 - $d = a$

Any questions?