 


TOTAL:
 CS150/EE141 = 50 pts
 EE241 = 60 pts

Homework 1: Solutions

Q1


a)



[5]

Note: exact cost estimates
not very important

b.)

 

[5]

NB: for both cases, the axes are not scaled. Therefore, cannot determine if slope is linear, quadratic, etc.

Q2

$$a.) T_A = \frac{5000}{1} \times \frac{1}{2 \times 10^9} = \underline{2.5 \mu s}$$

[2]

$$T_B = \frac{5000}{2} \times \frac{1}{1 \times 10^9} = \underline{2.5 \mu s}$$

$$b.) P_A = P_{\text{transistor}} \times N_{\text{transistor}}$$

$$= 2 \times 10^{-14} \times 1.2^2 \times 2 \times 10^9 \times 2 \times 10^6$$

$$= \underline{115.2 W}$$

[4]

$$P_B = 2 \times 10^{-14} \times 0.7^2 \times 1 \times 10^9 \times 4 \times 10^6$$

$$= \underline{39.2 W}$$

$$\begin{aligned}
 c.) E_A &= P_A \times T_A \\
 &= 115.2 \times 2.5 \times 10^{-6} \\
 &= \underline{288 \mu J}
 \end{aligned}$$

$$\begin{aligned}
 E_B &= P_B \times T_B \\
 &= 39.2 \times 2.5 \times 10^{-6} \\
 &= \underline{98 \mu J}
 \end{aligned}$$

[2]

d.) Batteries store fixed amount of energy. Therefore, B better, as it uses less energy. [2]

Q3.

a.)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

[4]

b.) It introduces a 1-cycle delay betw. the AND and OR gate. This means that Y is now the OR of the C input on this clock cycle and the AND of inputs A and B, from the previous cycle.

i.e. $Y = C \text{ OR } (A^{-1} \text{ AND } B^{-1})$,
 where X^{-1} means input X on the previous cycle.

[1]

Q4. [10]

a.) Logic synthesis: convert HDL into logical gate netlist (similar to logic diagram). Tool: Xilinx Synthesis Tool (XST)
 Partition/Map: divide circuit/netlist up into small partitions that can be implemented on individual LUTs or SLICES. Tool: Xilinx MAP.
 Place and Route: place partitions onto specific SLICES in the FPGA. Decide wire routing between SLICES. Tool: Xilinx PAR
 Create configuration bitstream: convert PAR'd design into a bit-file that will configure all LUTs and switching fabric correctly. Tool: Xilinx BitGen.
 Program FPGA: use Impact s/w and a hardware programmer (e.g. JTAG)

b.) Logic synthesis: convert HDL into a logical gate netlist. Tool: Design Compiler
 Map to standard cells: map the netlist onto standard cells. Tool: Design Compiler
 Place and route: place the standard cells, route the wires between them. Tool: IC Compiler
 Create mask: create a physical mask that can be used to etch the ASIC. Tool: done by fab
 Fabrication: use the masks to fabricate the ASIC. Tool: done by fab.

Q5

[4]

Let $C = \text{cost}$

$$C_{\text{ASIC}} = 10^6 + 3x$$

$$C_{\text{FPGA}} = 100x$$

$$\text{Cost crossover at : } 10^6 + 3x = 100x$$

$$97x = 10^6$$

$$x = 10309$$

$x < 10309$: use FPGAs

$x > 10309$: make an ASIC

Q6

[6]


```
module m(  
    input A,  
    input B,  
    input C,  
    output Y  
);  
    wire w1, w2;  
    xor(w1, A, B);  
    not(w2, C);  
    and(Y, w1, w2);  
endmodule
```

Q7

[5]

```
module m(  
    input A,  
    input B,  
    input C,  
    output Y  
);  
    assign Y = (A ^ B) & (~C);  
endmodule
```


Q8.

 

[6]

b.)

```

module oh-to-bin(
  input [7:0] oh-in,
  output [2:0] bin-out
);

```

```

  assign bin-out[0] = oh-in[7] | oh-in[5] | oh-in[3] | oh-in[1];

```

```

  assign bin-out[1] = oh-in[7] | oh-in[6] | oh-in[3] | oh-in[2];

```

```

  assign bin-out[2] = oh-in[7] | oh-in[6] | oh-in[5] | oh-in[4];

```

```

endmodule

```

[4]