



CS150 - EE141/241A

Fall 2014


Digital Design and Integrated Circuits

Instructors:

John Wawrzynek and Vladimir Stojanovic

Lecture 12


Outline

 


- ❑ Latch Design
- ❑ Register Design
- ❑ Setup, Hold and Clk-Q
- ❑ Race conditions

Latch versus Register (Flip-flop)

 
- ◆ **Latch: level-sensitive**
clock is low - hold mode
clock is high - transparent



 
- ◆ **Register: edge-triggered**
stores data when
clock rises



Characterizing Timing


 


Register

 

Latch

 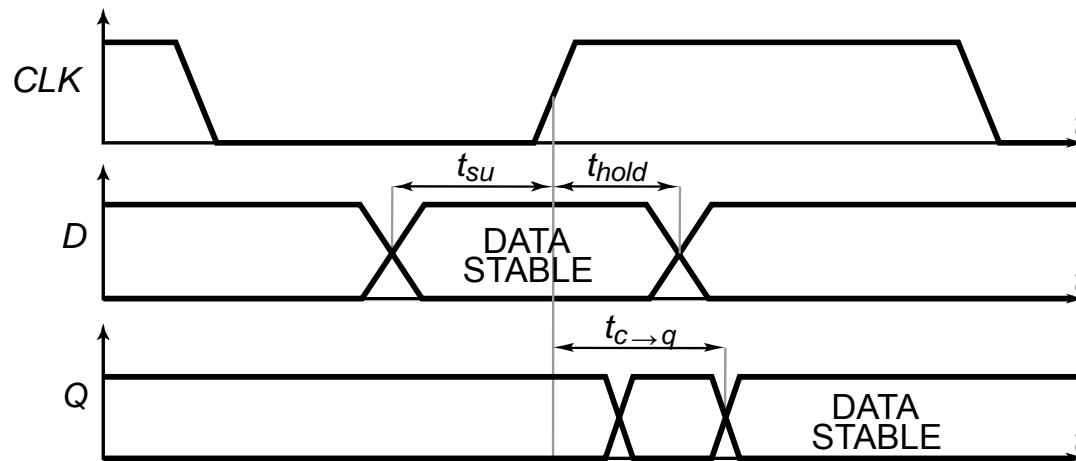Timing Definitions – Set-up and Hold Times










Latch Design

Storage Mechanisms


Static

  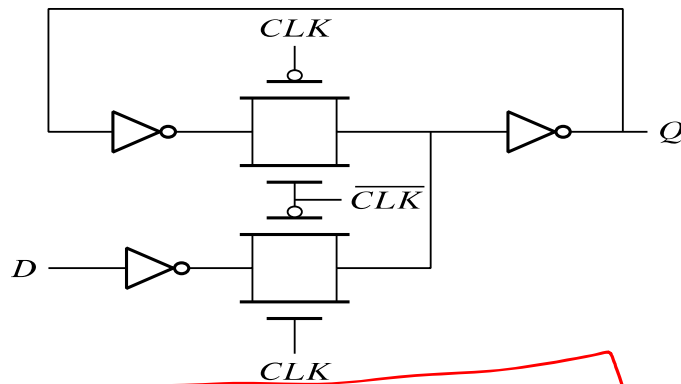

Dynamic

 
 


Basic Static Storage Element


 


- If D is high, D_b will be driven low
 - Which makes D stay high
- Positive feedback

Positive Feedback: Bi-Stability

  


Meta-Stability

  


Gain should be larger than 1 in the transition region

The Static Latch

 

Access transistor must be able to overpower the feedback

Writing a "1"

 


$$V_{dd} \xrightarrow{R_{on1}} \approx V_{dd} - V_{th} \quad R_{on1} \ll R_{on}$$

$\Delta V \uparrow \left. \vphantom{\Delta V} \right\} R_{on}$


$$\Delta V \ll V_{th} \quad R_{on1} \gg R_{on}$$

Addressing the write problem

 Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states



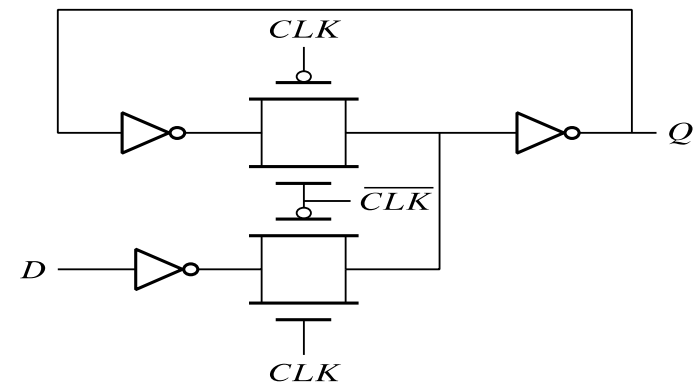
Forcing the state
(can implement as NMOS-only)



Converting into a MUX


Mux-Based Latches (pseudo-static)

Negative latch
(transparent when CLK= 0)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot D$$

Positive latch
(transparent when CLK= 1)

 

$$Q = \overline{Clk} \cdot Q + Clk \cdot D$$


Mux-Based Latch

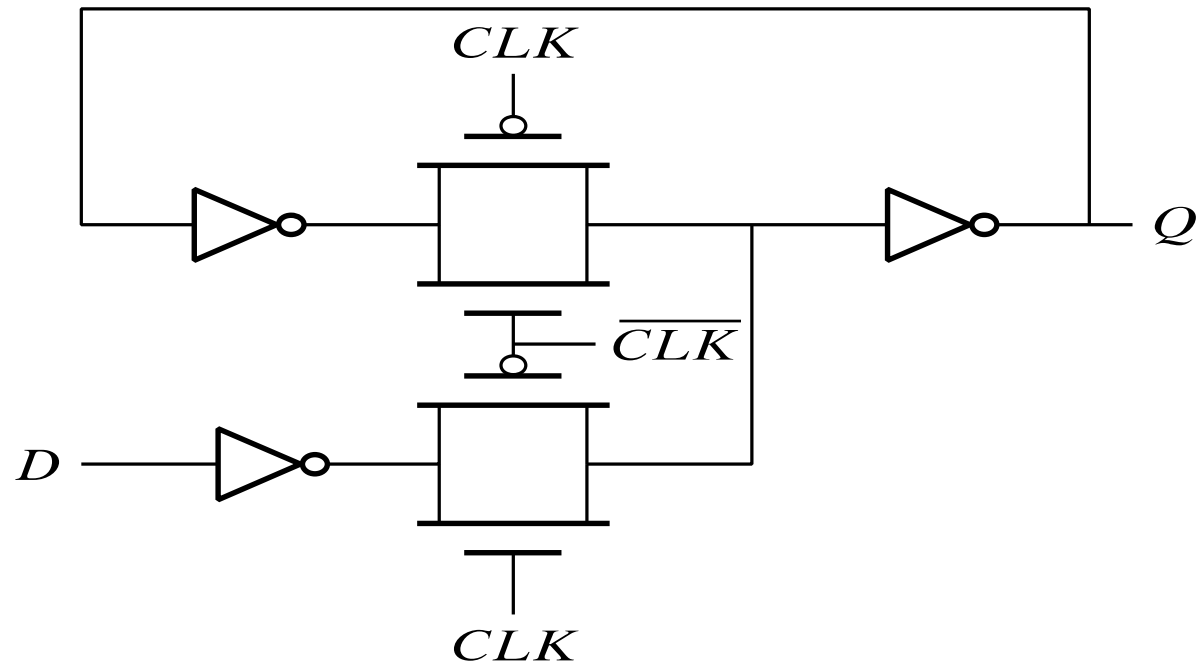



Register Design



Master-Slave Register (Edge-Triggered)

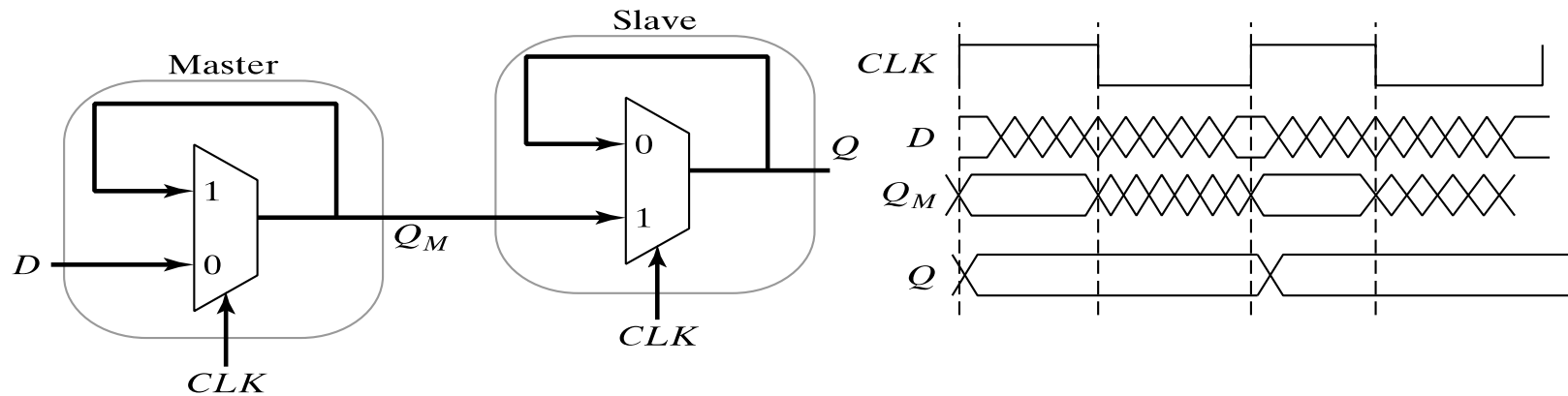


Two opposite latches trigger on edge
Also called master-slave latch pair

Master-Slave Register


Multiplexer-based latch pair

 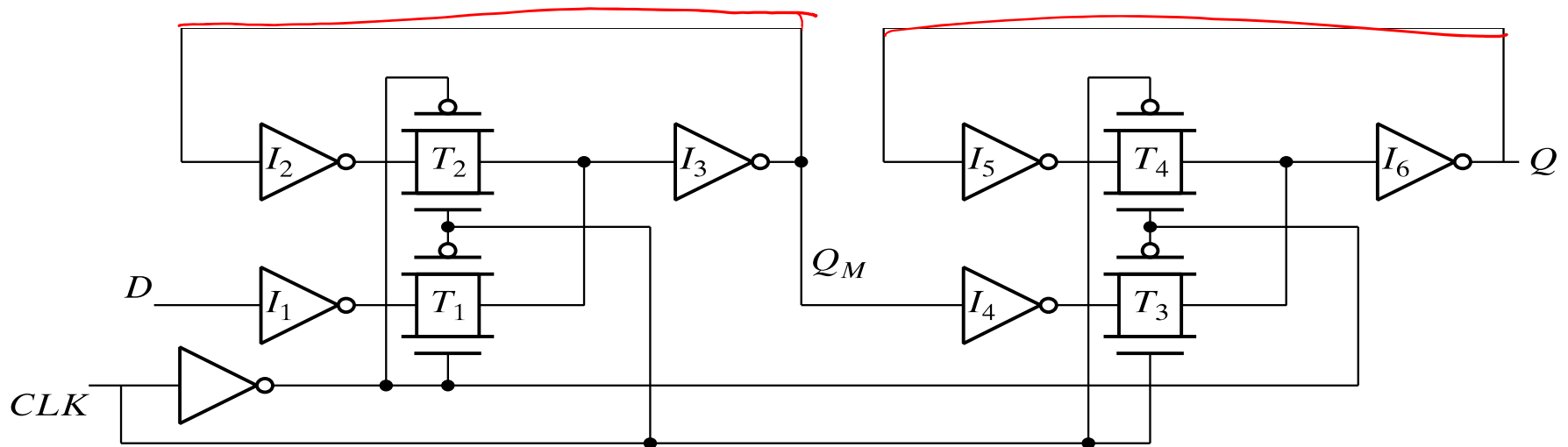

Pass-gate Dynamic MS Register

 


 - ❑ State stored on caps – no feedback
- ❑ Faster than static, but risky due to leakage and coupling




Setup, Hold, Clk-Q


Clk-Q Delay

 

Setup Time

 


(a) $T_{setup} = 0.21$ ns

 


(b) $T_{setup} = 0.20$ ns

More Precise Setup Time

 


Setup-Hold Time Illustrations

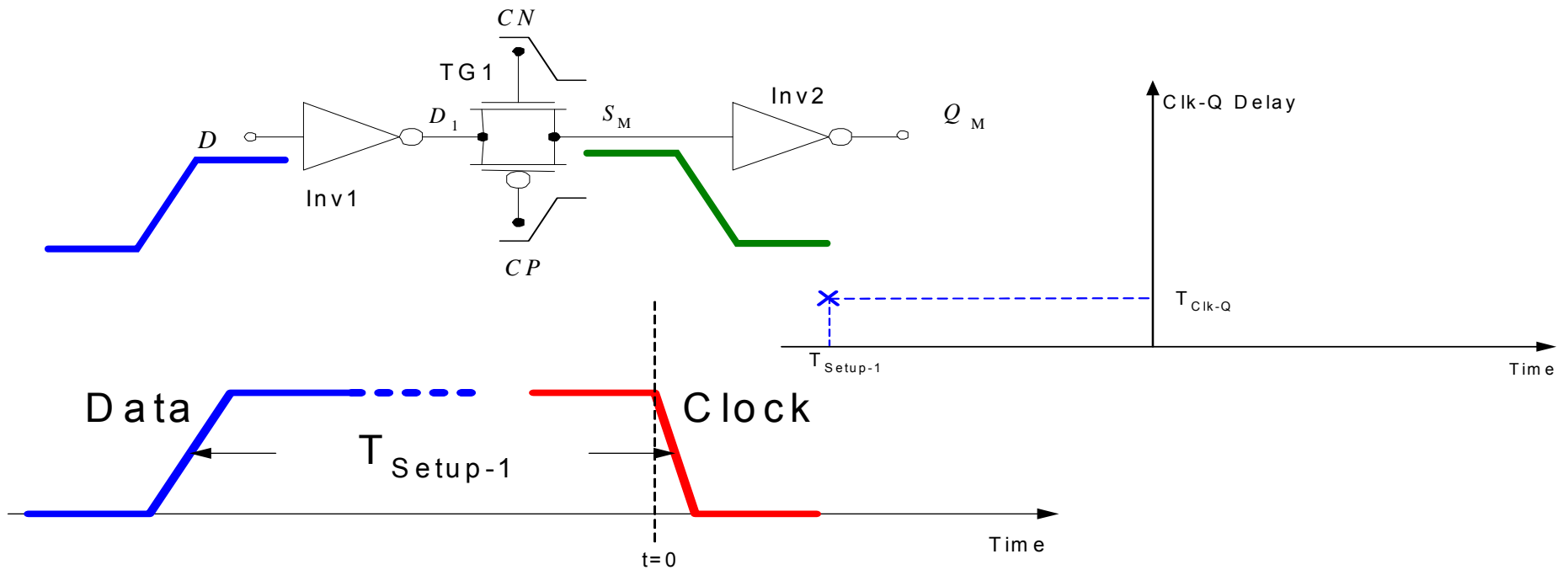Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

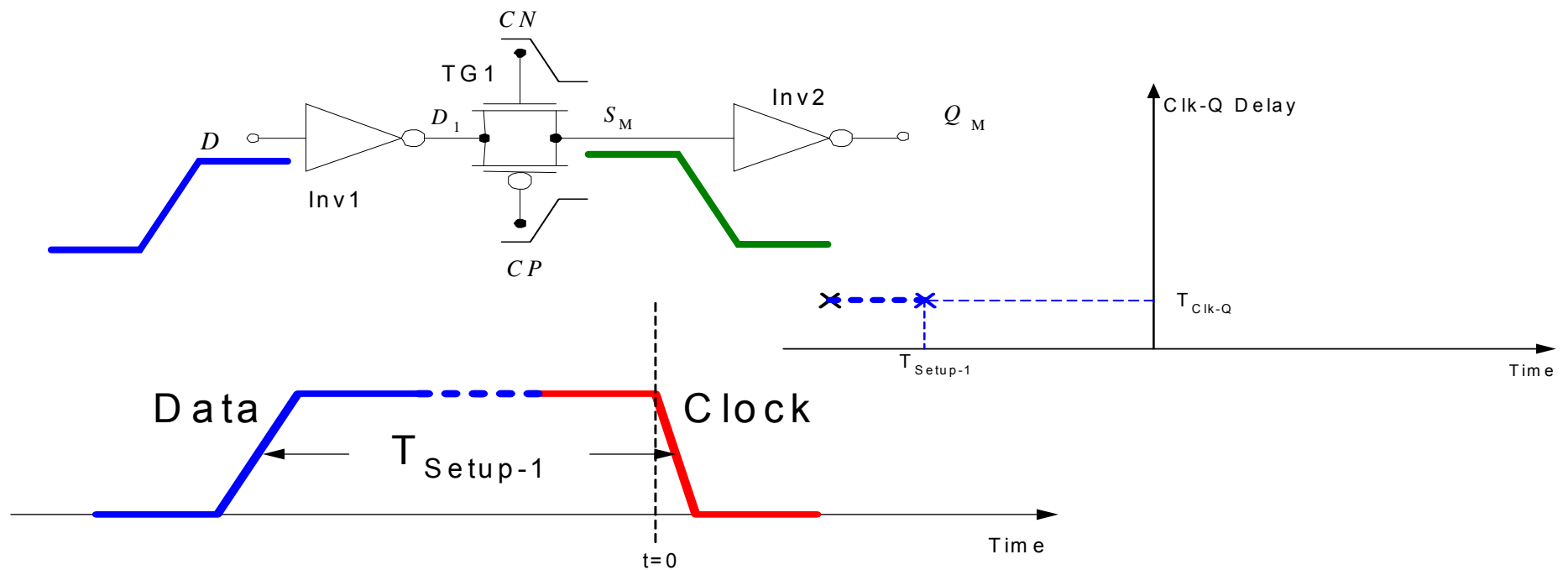Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

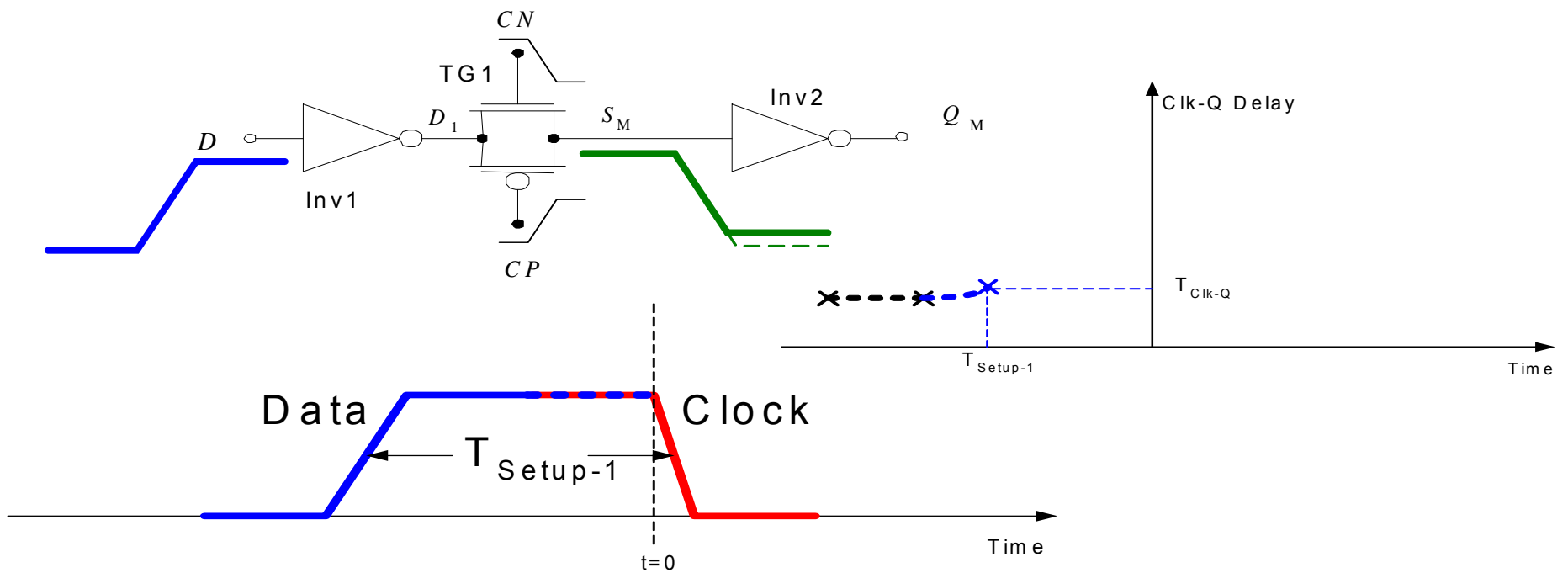Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

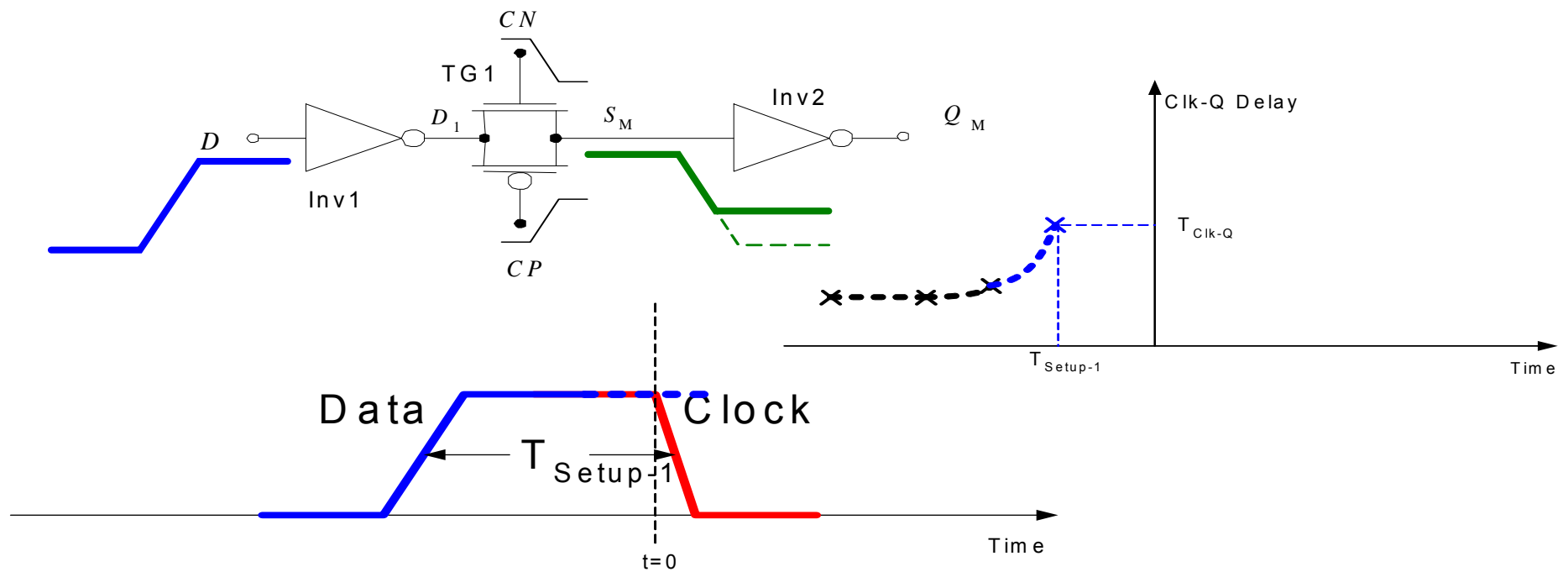Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

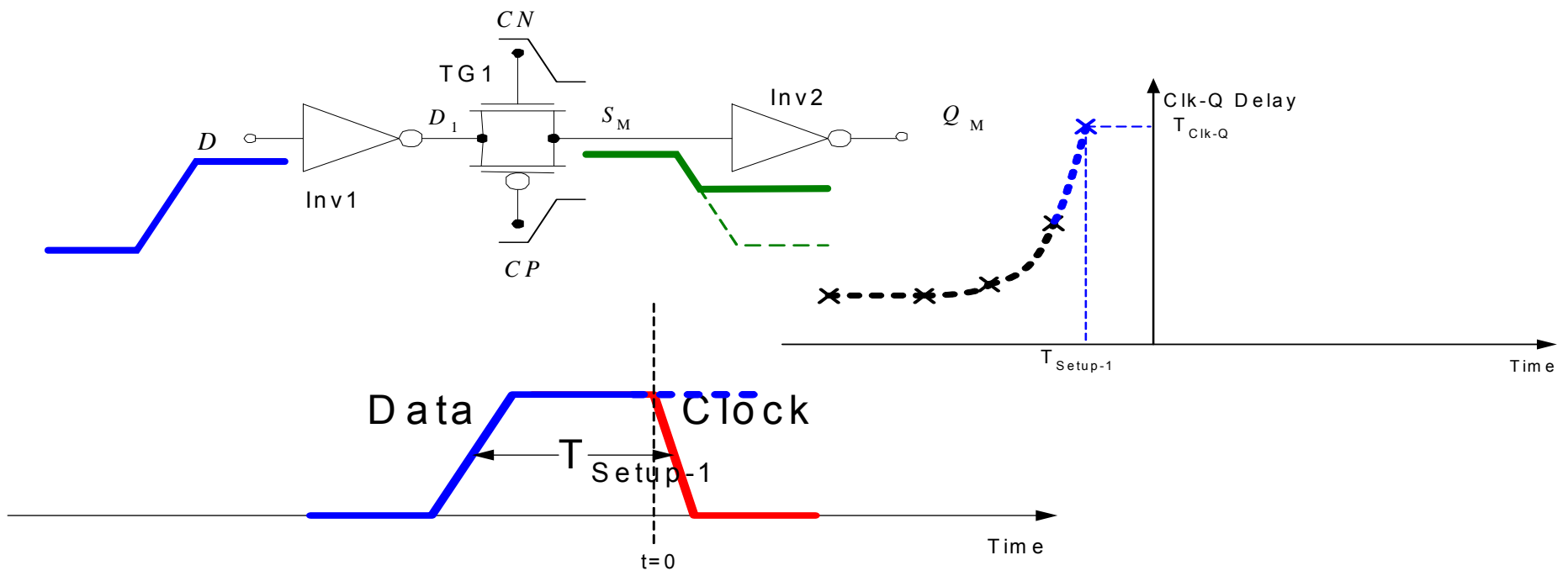Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

Hold-1 case

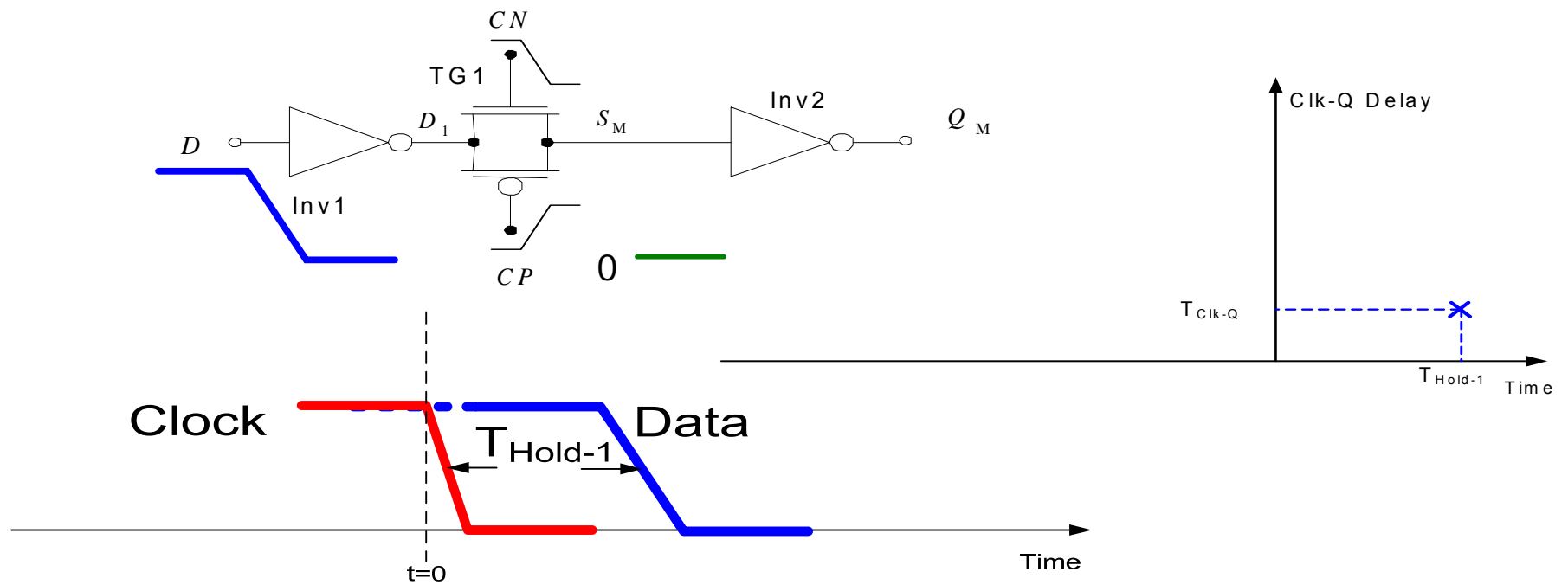


Setup-Hold Time Illustrations

Hold-1 case

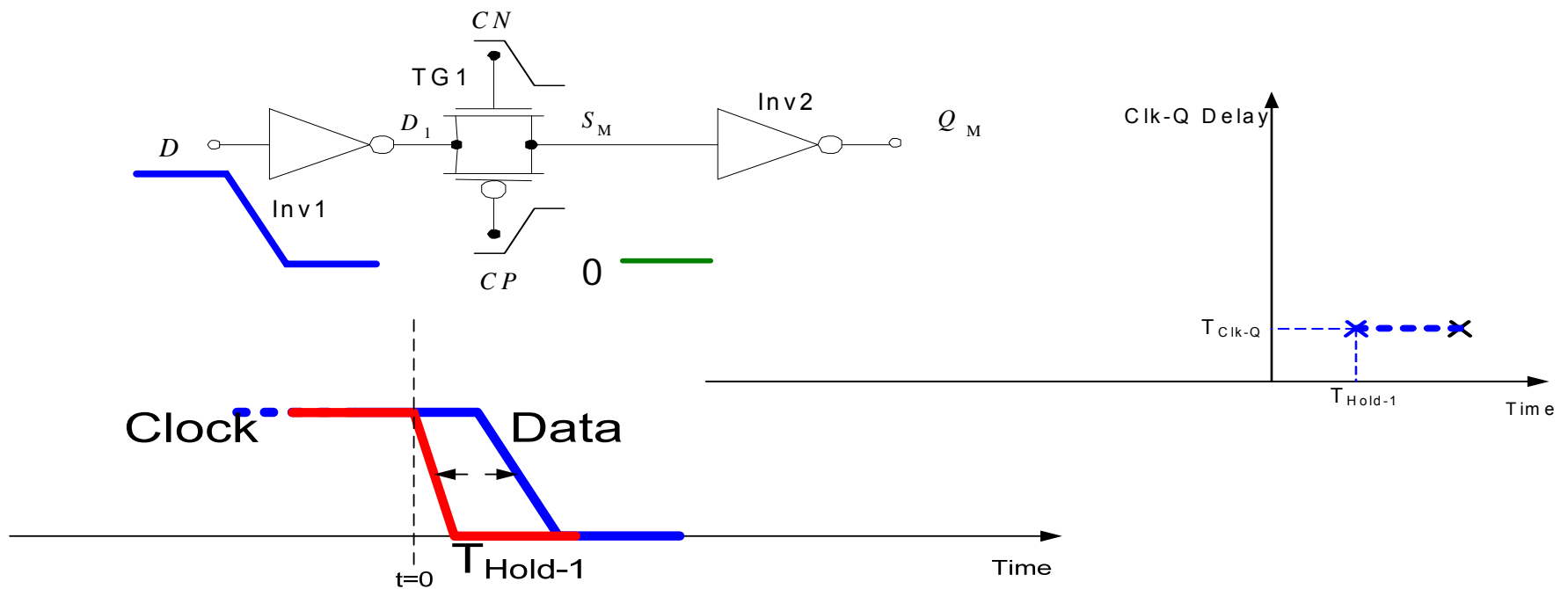


Setup-Hold Time Illustrations

Hold-1 case

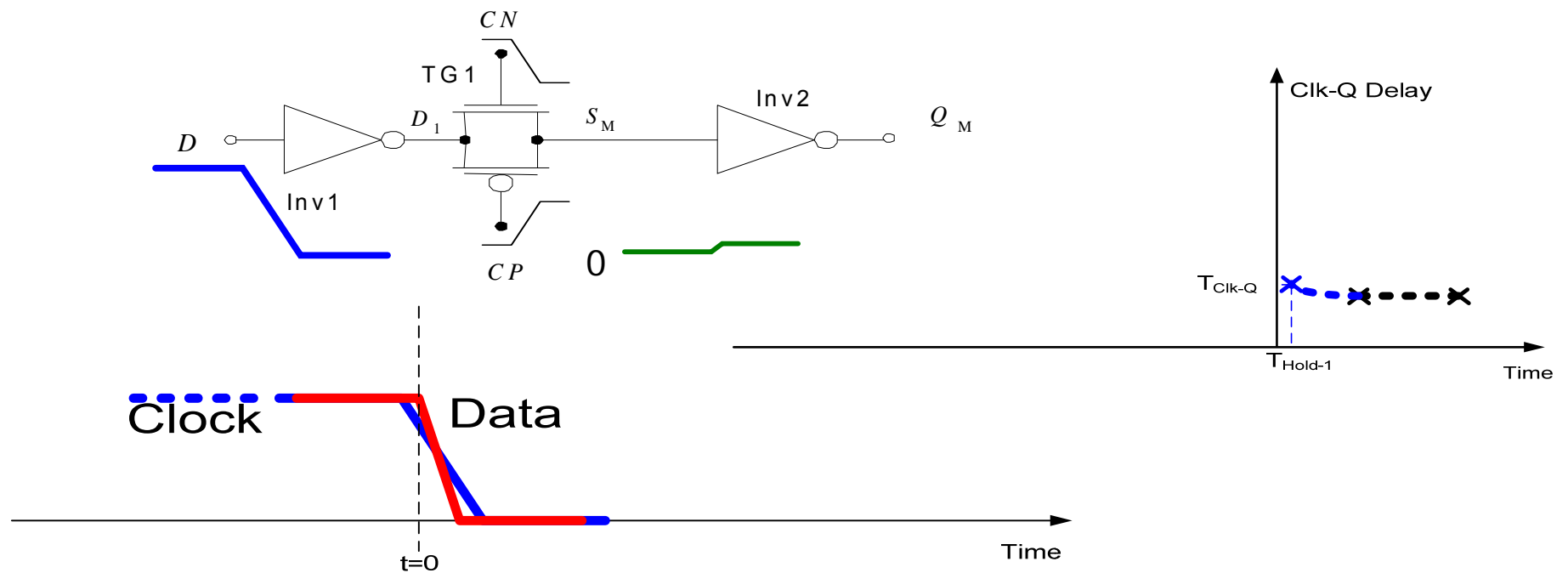


Setup-Hold Time Illustrations

Hold-1 case

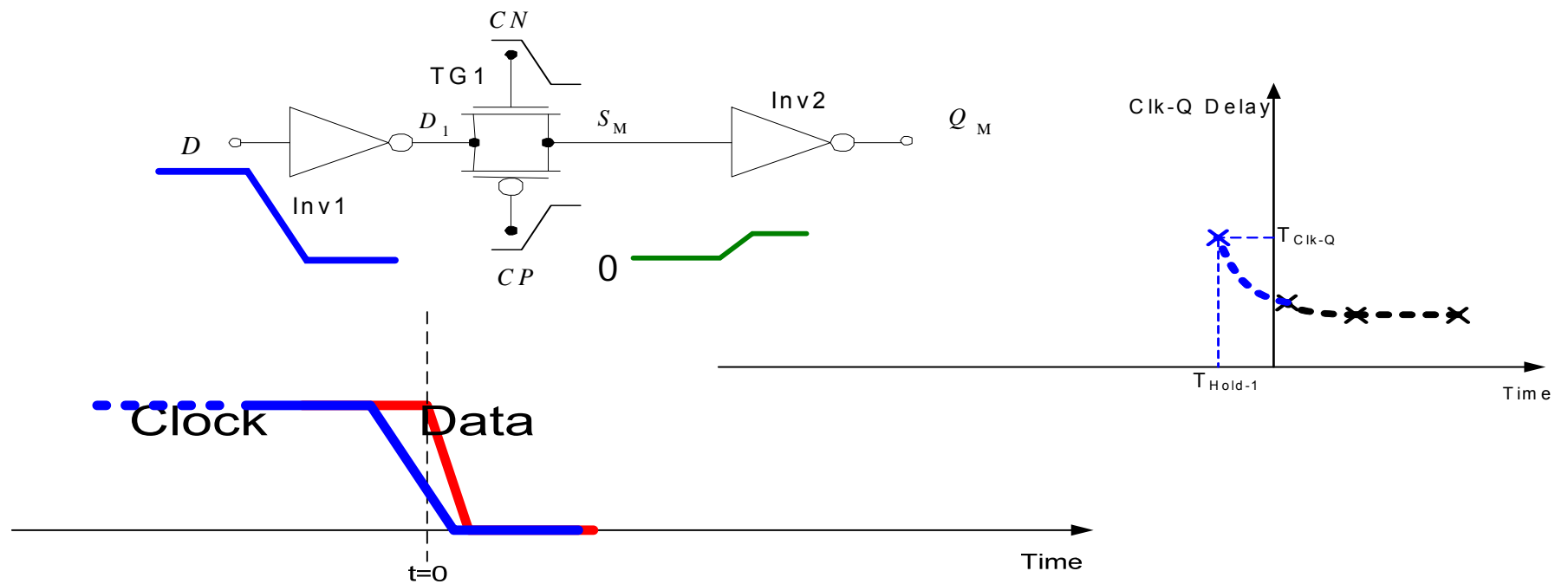

Setup-Hold Time Illustrations


Hold-1 case

 





Race conditions

Pass-gate MS Register

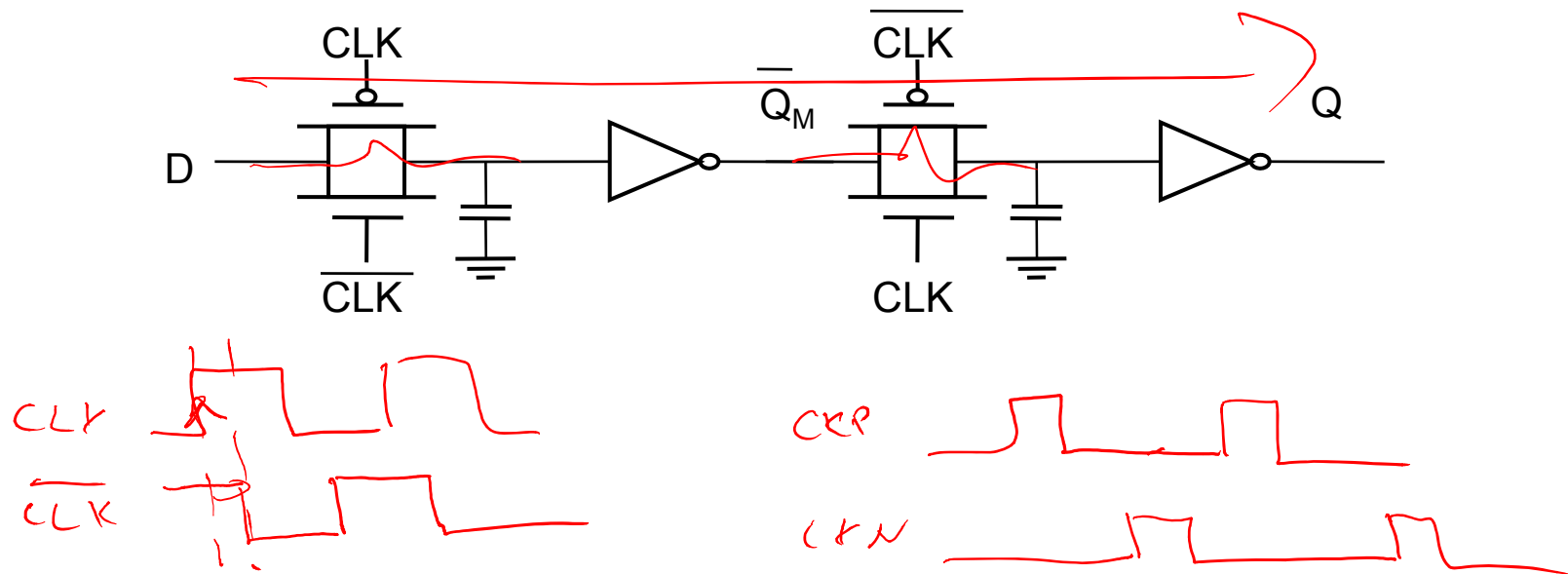

- ❑ Only works with non-overlapping clocks
- ❑ Race-through condition with overlapping clocks

Other Latches/Registers: C^2MOS

 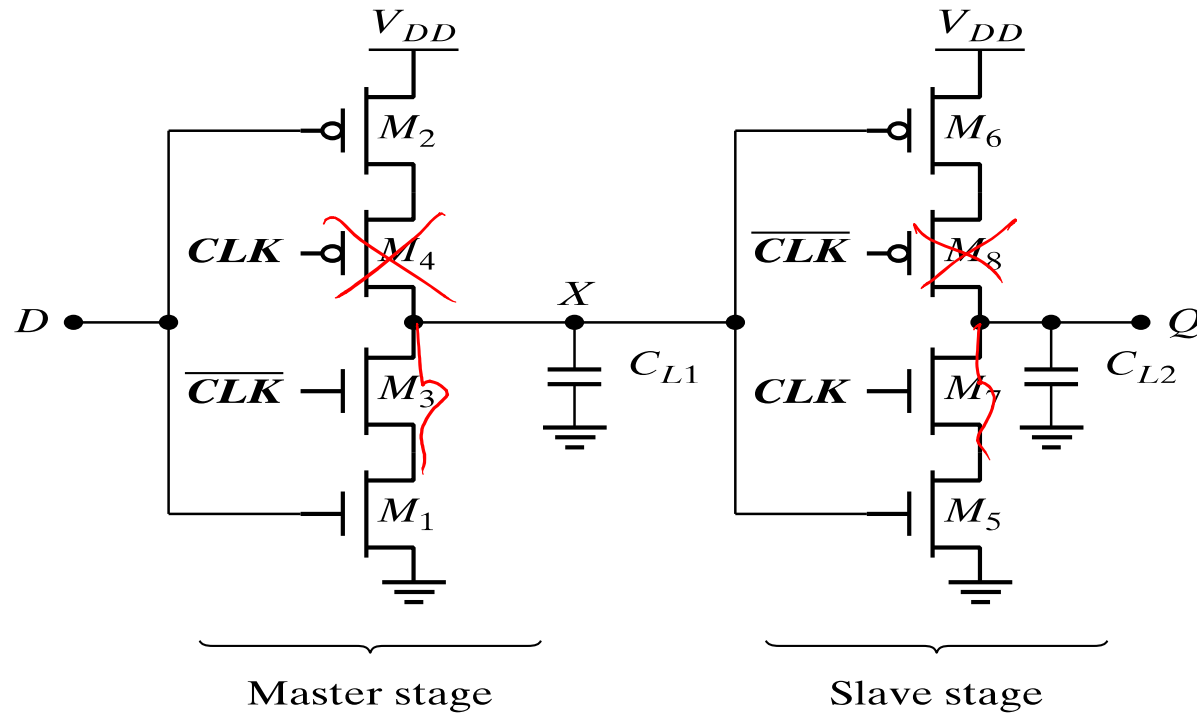

C²MOS – No Races

Latch-Based Design

- ◆ N latch is transparent when $\Phi = 0$

- ◆ P latch is transparent when $\Phi = 1$

