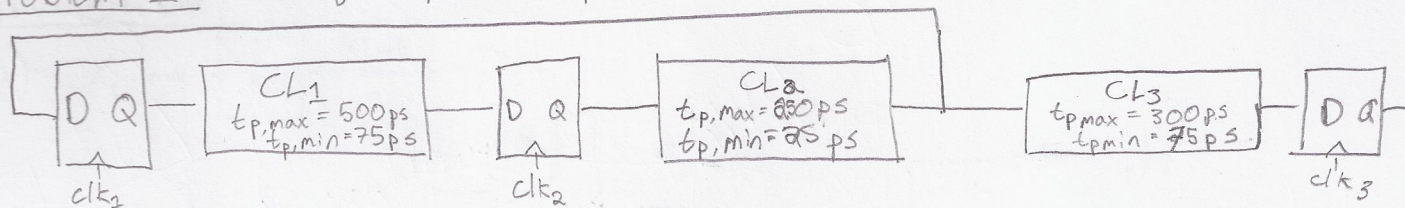


Homework 11

Kevin Chau
23816929
cs150-bd

Problem 1 $t_{clk-q} = 50ps$ $t_{setup} = 100ps$ $t_{hold} = 100ps$



a) no clock skew

$$T_{clock} > T_{clk-q} + T_{logic,max} + T_{setup} = (50ps) + (300ps) + (250ps) + (100ps) = \boxed{700ps}$$


hold time: $T_{hold} < T_{clk-q,min} + T_{logic,min}$ ← condition for no violation

since $T_{clk-q,min} + T_{logic,min} = 50ps + 25ps = 75ps < T_{hold} = 100ps$

there is a hold time violation.

$$T_{hold} \neq T_{ca} + T_{logic,min}$$

b) $T_{inv} = 50ps \pm 5ps$

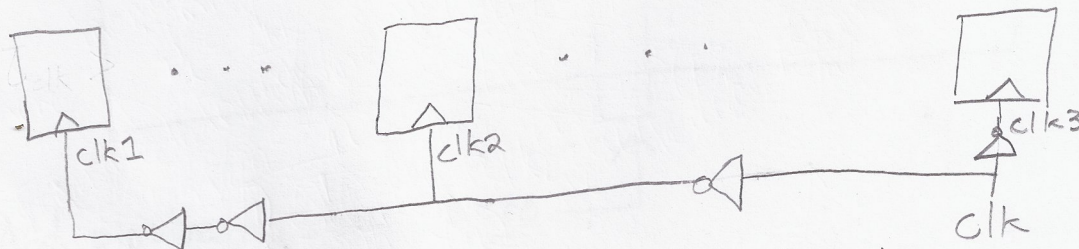

clk2 and clk3 are delayed by at most 55ps each.

clk1 has a maximum delay of 110ps (2 inverters)

$$\text{critical path} = t_{ca} + t_{logic,max} + T_{setup} + T_{skew,max} \\ = 50ps + 500ps + 100ps + 110ps = 760ps$$

$$\boxed{t_{clk} > 760ps}$$

c) condition: $t_{hold} + t_{skew} < t_{ca,min} + t_{logic,min}$

but $t_{hold} + t_{skew} = 100 + 110 \not< 50ps + 25$

so we must add a delay to logic block #2 in order to avoid a race. The minimum delay necessary


is $210 - 50ps - 25ps = t_{hold} + t_{skew} - t_{ca} - t_{logic,min} \\ = 135ps$

$$\boxed{t_{delay} \geq 135ps}$$

Add the delay between register 1 & 2


$$y_i = a * y_{i-1} + b * x_i + c * x_{i-1}$$

Problem 2

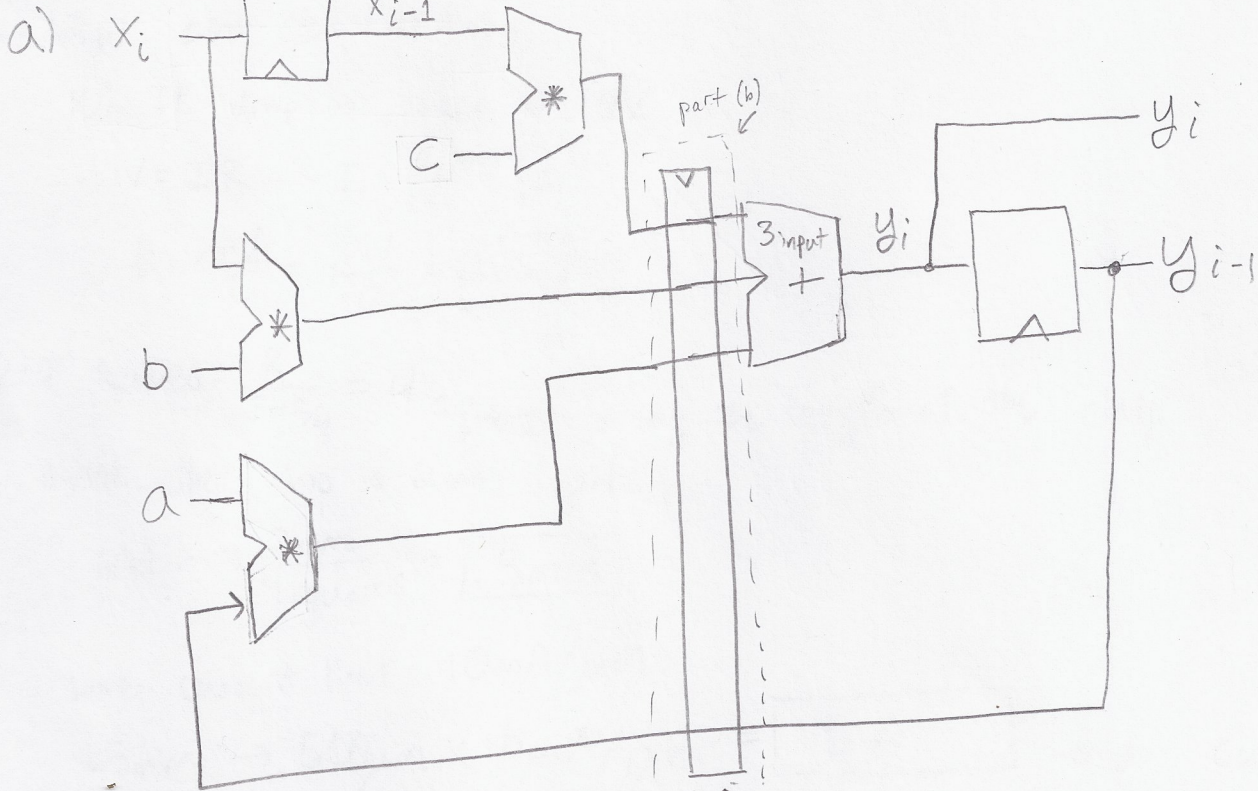

b) Add pipeline registers here

c) $y_{i+1} = a * y_i + b * x_{i+1} + c * x_i$

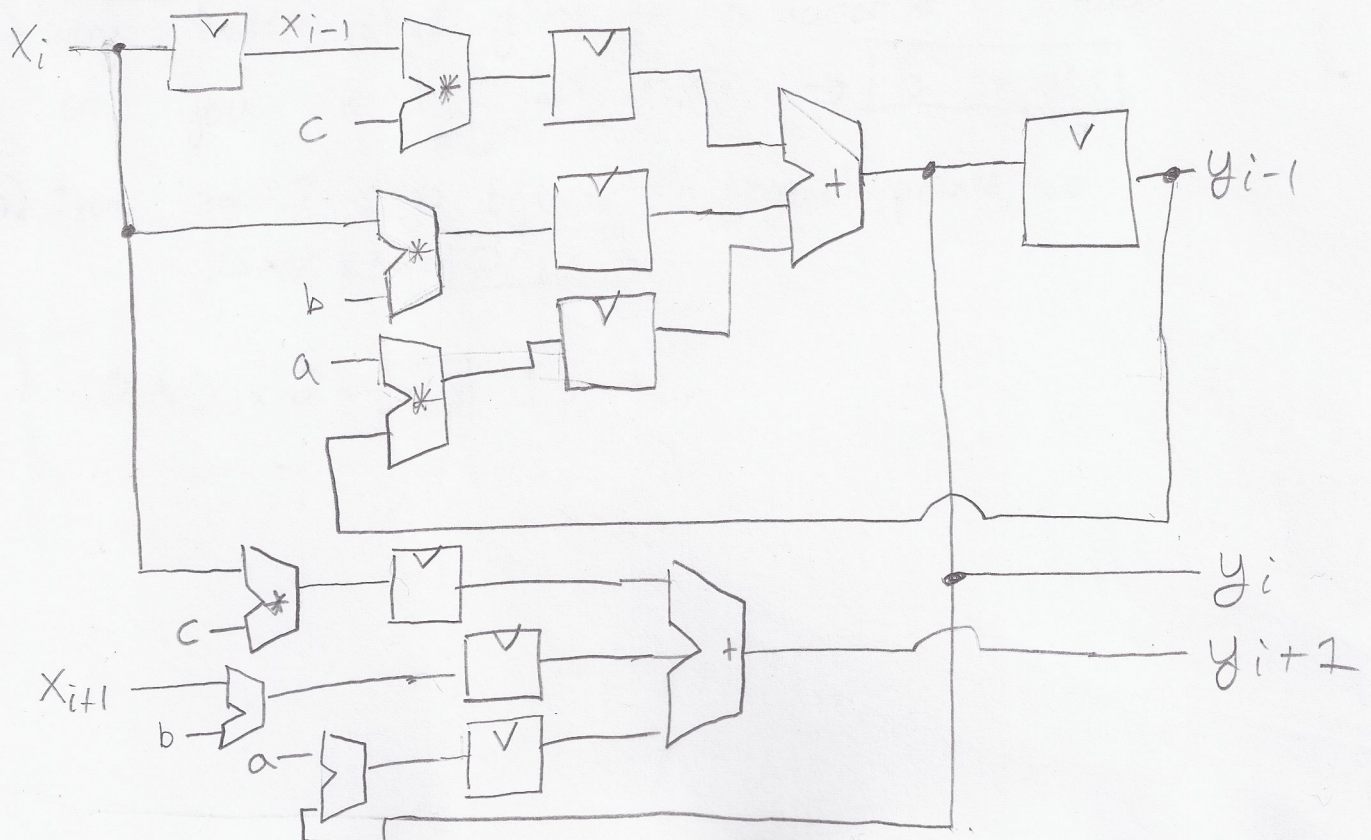

Problem 3

a) 12W CPU @ 1.2V = V_{dd}

10% IR drop $\rightarrow .1 \times 1.2V = .12V$

$$.12V = IR \quad I = \frac{12W}{1.2V} = 10A$$

$$R = \frac{.12V}{I} = \frac{.12V}{10} = \boxed{12m\Omega}$$

b) # squares = $\frac{R}{3m\Omega/sq} = 4$ squares along the length of the chip
since the chip is 2mm wide,

$$\text{width} = \frac{2mm}{4 \text{ squares}} = \boxed{.5mm}$$

c) wire current limit 10mA/ μm

$$.5mm \rightarrow 500\mu m \times 10mA/\mu m = \boxed{5A} \text{ Max current}$$

$$d) \frac{10A}{10 \frac{mA}{\mu m}} = 1000\mu m = \boxed{1mm}$$

Problem 4

a) Every buffer stage gives you a factor of 4 increase
so you need $4^5 = 1024 \rightarrow \boxed{5 \text{ stages}}$

b) There are 8 stages between the diagonal points, so
 $.05 \times 50 \times 8 = \boxed{20ps}$

$$c) .05 \times 50 \times 2 = \boxed{5ps}$$